

# Digital Level Shifter for I<sup>2</sup>S Interfaces

## UPP-B2 and UPV-B41

### Application Note

#### Products:

- R&S®UPP200
- R&S®UPP400
- R&S®UPP800
- R&S®UPP-B2
- R&S®UPP-B4
- R&S®UPV
- R&S®UPV-B41

This application note proposes a digital level shifter for connecting the I<sup>2</sup>S interfaces R&S®UPP-B2 and R&S®UPV-B41 to devices under test with a logic voltage different from 3.3 V.

#### Note:

Please find the most up-to-date document on our homepage <http://www.rohde-schwarz.com/appnote/1GA71>.

# Table of Contents

<b>1</b>	<b>Background</b> .....	<b>3</b>
1.1	Logic voltage.....	3
1.2	I <sup>2</sup> S interface .....	3
1.1	I <sup>2</sup> S interface options on R&S®UPV and R&S®UPP.....	3
1.2	Pin assignments .....	3
1.2.1	UPP-B2 and UPV-B41 .....	3
1.2.2	UPP-B4.....	4
<b>2</b>	<b>Design of the Level Shifter</b> .....	<b>5</b>
2.1	General.....	5
2.2	Bill of materials .....	5
2.3	Circuit diagram.....	6
2.4	Testing .....	6
<b>3</b>	<b>Literature</b> .....	<b>7</b>
<b>4</b>	<b>Ordering Information</b> .....	<b>8</b>

# 1 Background

## 1.1 Logic voltage

Logic circuits can have different logic voltages, depending on the semiconductor technology applied. TTL circuits have 5 V logic voltage. Standard CMOS circuits usually have 3.3 V logic voltage.

## 1.2 I<sup>2</sup>S interface

The I<sup>2</sup>S (Inter-IC Sound) interface is a serial bus for audio data, originally specified by Philips Semiconductors (Philips Semiconductors, February 1986). The bus was introduced for digital audio connection between different ICs. It comprises one data line and two control lines (clock and word select).

Originally 5 V TTL logic voltage was specified, but the specification was planned to be extended to upcoming other logic voltages. The specification has never been extended, but in practice it is used independent of the logic voltage.

## 1.1 I<sup>2</sup>S interface options on R&S<sup>®</sup>UPV and R&S<sup>®</sup>UPP

For audio analyzers R&S<sup>®</sup>UPV and R&S<sup>®</sup>UPP there are I<sup>2</sup>S interface options R&S<sup>®</sup>UPV-B41, R&S<sup>®</sup>UPV-B42, R&S<sup>®</sup>UPP-B2 and R&S<sup>®</sup>UPP-B4 available.

R&S<sup>®</sup>UPV-B42 is the most versatile interface available with parameters extending far beyond the I<sup>2</sup>S functionality. This interface also provides a probe, which can be connected to the device under test with very short data lines. The probe also provides a parameter to select the logic voltage between the values 0.9 V, 1.2 V, 1.5 V, 1.8 V, 2.5 V and 3.3 V.

All other I<sup>2</sup>S interfaces on Rohde & Schwarz audio analyzers have a fixed logic voltage of 3.3 V.

## 1.2 Pin assignments

### 1.2.1 UPP-B2 and UPV-B41

The pin assignments of the I<sup>2</sup>S interfaces on UPP-B2 and UPV-B41 are compatible.

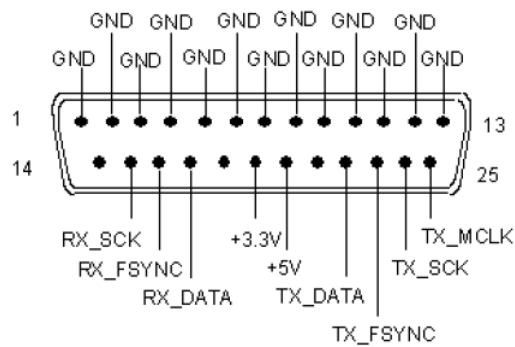


Fig. 1-1: Pin assignment of the I<sup>2</sup>S interface of UPP-B2 and UPV-B41

Therefore the same level shifter design can be used with both instruments. The exemplary implementation shown in this application note is compliant with this pinout.

## 1.2.2 UPP-B4

The I<sup>2</sup>S interface of UPP-B4 has four TX data lines and four RX data lines with common TX control lines and common RX control lines. It uses a 26-pin Sub-D-HD connector.

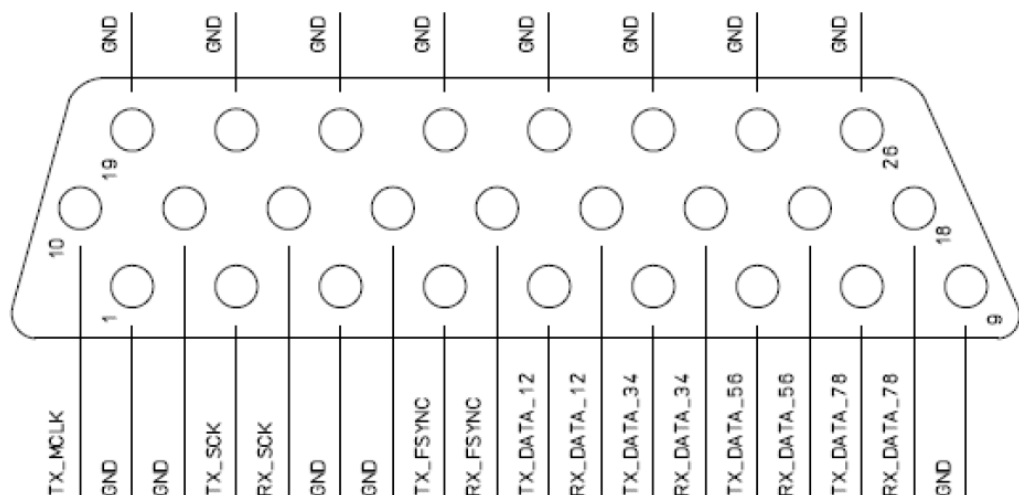


Fig. 1-2: Pin assignment of the I<sup>2</sup>S interface of UPP-B4

A level shifter with complete support for this interface requires 7 TX (high-to-low) and 6 RX (low-to-high) buffers. Consequently four pieces of the logic level shifter SN74LV4T125 are required. The design principle, however, is the same as with the circuit diagram shown in this application note.

## 2 Design of the Level Shifter

### 2.1 General

The design uses standard CMOS level shifter ICs. The circuit is powered from the 3.3 V output pin of the audio analyzer's I<sup>2</sup>S interface. The interface ICs require a supply voltage equal to the lower logic level, which is obtained using a simple low dropout linear regulator.

The level shifter buffers provide enable inputs for each buffer. When the buffer is disabled, its output has high impedance which allows to connect multiple outputs to one bus. In the present design the buffers are always enabled, as is the case with the I<sup>2</sup>S outputs of the R&S<sup>®</sup> audio analyzers.

The supply voltage inputs of the ICs and the output of the linear regulator are provided with 100 nF blocking capacitors.

The circuit allows a compact implementation, which can be installed in a Sub-D adapter case.

### 2.2 Bill of materials

The following is a list of required materials in addition to a printed wiring board or prototype board and some wires. The specific types are examples. Equivalent types from other manufacturers can also be used. If a logic voltage different from 1.8 V is desired, replace the low dropout regulator with an appropriate type for the desired voltage.

No.	Qty.	Designation	Type	Manufacturer
1	2	Single Power Supply Quadruple Buffer Translator GATE With 3-State Output CMOS Logic Level Shifter	SN74LV4T125	Texas Instruments
2	1	1.8 V 300 mA CMOS Low Dropout Regulator	NCV8114ASN180	ON Semiconductor
3	4	Multilayer ceramic capacitor 100 nF 16 V X7R		Murata
4	1	Sub-D connector female 25 pins		
5	1	Sub-D connector male 25 pins		
6	1	Adapter case for 25 pin D-Sub connectors	DPAK-M-25-K	encitech

Table 2-1: Bill of Materials

## 2.3 Circuit diagram

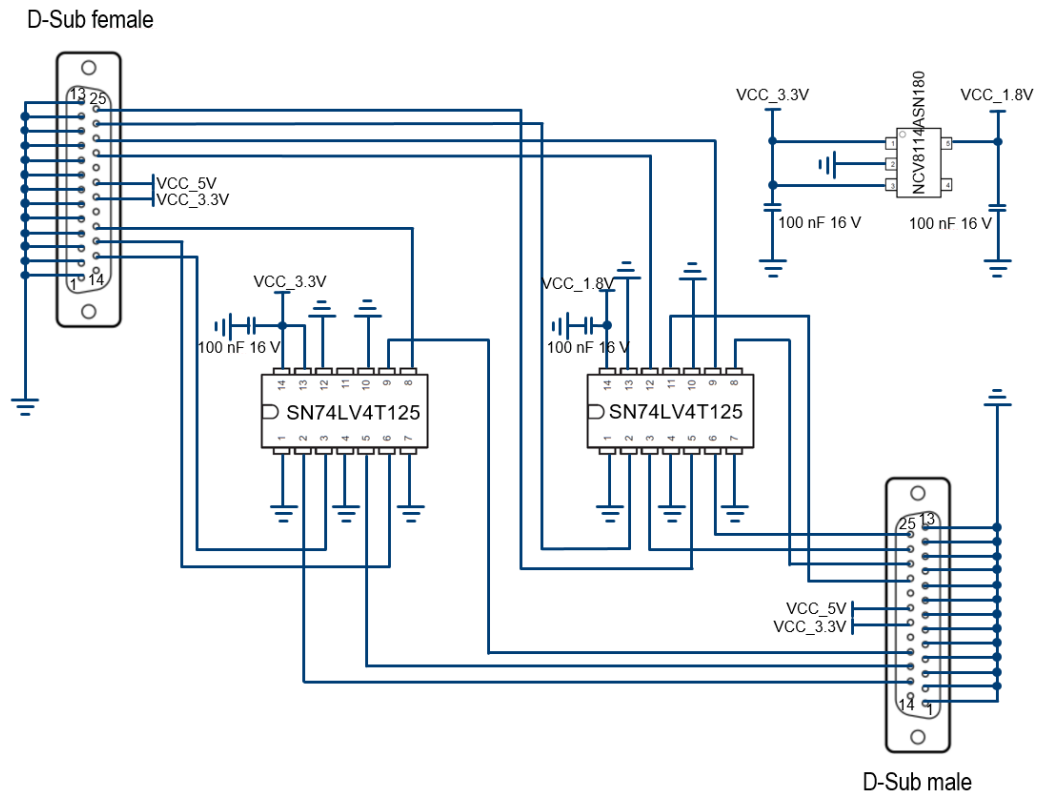


Fig. 2-1: Circuit diagram of the I<sup>2</sup>S logic level shifter

## 2.4 Testing

For testing it is useful to make a female connector which loops the TX data lines of the interface to the RX connections. This way the signals are converted from 3.3 V logic level to the lower logic level (e.g. 1.8 V) and back.

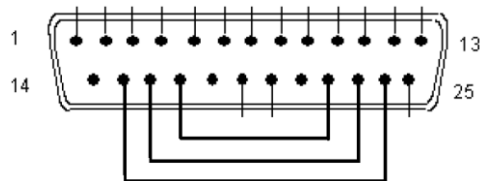


Fig. 2-2: Circuit diagram for loop test plug

Configure the I<sup>2</sup>S generator and analyzer identically, preferably at the highest available sample rate and word length. Generate a 1 kHz sine signal at 0 dBFS and check the THD+N value.

The signals at the low logic level can be tapped with oscilloscope probes to check the signal quality. For a detailed analysis of the interface signals you can make advantage of the I<sup>2</sup>S triggering and decoding software available for the oscilloscopes R&S® RTO2000, R&S® RTE1000, R&S® RTA4000 and R&S® RTM3000.

## 3 Literature

- [1] **ON Semiconductor** NCV8114 Product Preview - 300 mA CMOS Low Dropout Regulator. - [s.l.] : Semiconductor Components Industries, LLC, December 2016.
- [2] **Philips Semiconductors** I<sup>2</sup>S bus specification. - February 1986.
- [3] **Texas Instruments** SN74LV4T125 Single Power Supply Quadruple Buffer Translator GATE With 3-State Output CMOS Logic Level Shifter. - [s.l.] : Texas Instruments, September 2014.

## 4 Ordering Information

Designation	Type	Order No.
Audio Analyzer two channels	R&S®UPP200	1411.1003.02
Audio Analyzer four channels	R&S®UPP400	1411.1003.04
Audio Analyzer eight channels	R&S®UPP800	1411.1003.08
Digital audio interfaces AES/EBU, S/P DIF, I2S	R&S®UPP-B2	1411.2300.02
Audio analyzer, analog interfaces, DC to 250 kHz	R&S®UPV	1146.2003.02
I2S interface for standard measurements	R&S®UPV-B41	1146.5402.02
I2S oscilloscope software	R&S®RTO-K5	1329.7302.02
I2S oscilloscope software	R&S®RTE-K5	1326.1210.02
I2S oscilloscope software	R&S®RTA-K5	1335.7723.02
I2S oscilloscope software	R&S®RTM-K5	5710.0882.02



## Rohde & Schwarz

The Rohde & Schwarz electronics group offers innovative solutions in the following business fields: test and measurement, broadcast and media, secure communications, cybersecurity, radiomonitoring and radiolocation. Founded more than 80 years ago, this independent company has an extensive sales and service network and is present in more than 70 countries.

The electronics group is among the world market leaders in its established business fields. The company is headquartered in Munich, Germany. It also has regional headquarters in Singapore and Columbia, Maryland, USA, to manage its operations in these regions.

## Regional contact

Europe, Africa, Middle East  
+49 89 4129 12345  
[customersupport@rohde-schwarz.com](mailto:customersupport@rohde-schwarz.com)

North America  
1 888 TEST RSA (1 888 837 87 72)  
[customer.support@rsa.rohde-schwarz.com](mailto:customer.support@rsa.rohde-schwarz.com)


Latin America  
+1 410 910 79 88  
[customersupport.la@rohde-schwarz.com](mailto:customersupport.la@rohde-schwarz.com)

Asia Pacific  
+65 65 13 04 88  
[customersupport.asia@rohde-schwarz.com](mailto:customersupport.asia@rohde-schwarz.com)

China  
+86 800 810 82 28 | +86 400 650 58 96  
[customersupport.china@rohde-schwarz.com](mailto:customersupport.china@rohde-schwarz.com)
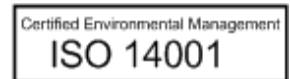
## Sustainable product design

- Environmental compatibility and eco-footprint
- Energy efficiency and low emissions
- Longevity and optimized total cost of ownership



This and the supplied programs may only be used subject to the conditions of use set forth in the download area of the Rohde & Schwarz website.

Version 1GA71\_0e | R&S® Digital Level Shifter for I<sup>2</sup>S Interfaces UPP-B2 and UPV-B41 Digital Level Shifter for I<sup>2</sup>S Interfaces UPP-B2 and UPV-B41

R&S® is a registered trademark of Rohde & Schwarz GmbH & Co. KG; Trade names are trademarks of the owners.

### Rohde & Schwarz GmbH & Co. KG

Mühlhofstraße 15 | 81671 Munich, Germany

Phone + 49 89 4129 - 0 | Fax + 49 89 4129 - 13777

[www.rohde-schwarz.com](http://www.rohde-schwarz.com)