

Measuring power-on behavior of LLC resonant converters

LLC¹⁾ resonant converters achieve very high efficiency levels due to soft switching. However, during the power-on phase such a converter might behave differently until the controller has reached a steady state. Measuring the inrush current and the power-on time ensures that they are within standards and comply with the data sheet.

¹⁾ Named after the typical converter structure of two inductances L and one capacitance C.

Your task

Verifying power converter behavior under various conditions such as load changes and power-on are important tasks to ensure reliable operation in the actual application. Inrush currents and power-on time are critical parameters. If the inrush current exceeds certain levels, fuses in the electrical installation network might blow. Power-on time is usually an important specification of a DC/DC converter.

T&M solution

A typical power-on duration of a power converter can be rather long, often several 100 ms. An oscilloscope with deep memory is required to capture such a long time interval and still have enough time resolution to see switching behavior in detail. The R&S®RTM3000, the R&S®RTA4000, the R&S®RTE1000 and the R&S®RTO2000 oscilloscopes provide up to 200 Msample or 1 Gsample of acquisition memory. Combined with their flexible zoom functionality and automatic measurement functions, they are a good choice for these applications.

While the switching frequencies of an LLC resonant converter are in the range of only around 100 kHz, the fast rise/fall times of the switches make high measurement bandwidth necessary¹⁾. High voltage differential probes like the R&S®RT-ZHD probes offer bandwidth up to 200 MHz, which makes them ideal for this kind of application. They also provide a particularly high DC offset compensation range independent from the oscilloscope, which makes them valuable for DC link ripple voltage measurements as well.


Measurement setup

A commercially available 230 V to 24 V DC power supply for industrial applications is used as the device under test (DUT). The LLC converter consists of a power factor correction (PFC) stage and the actual LLC converter (see figure below).

¹⁾ Given rise/fall times of signals, the bandwidth can be estimated using

$$f_{BW} = 0.35 \times \frac{1}{t_{rise(10-90)}}$$

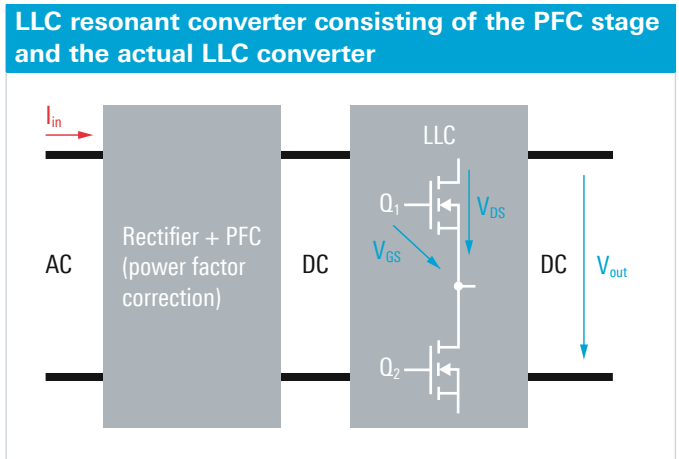E.g. GaN MOSFETs may exhibit $t_r < 5 \text{ ns} \leftrightarrow f_{BW} > 70 \text{ MHz}$.



The measurement is performed with an R&S®RTO2000 oscilloscope. The results are shown in the figure below. Two R&S®RT-ZHD16 high voltage differential probes are used to measure V_{GS} and V_{DS} of Q_1 (yellow and green). The inrush current is measured with an R&S®RT-ZC20B current probe, and the output voltage with an R&S®RT-ZP10 passive probe (orange and blue). An electronic load regulates the delivered output power. A frequency measurement versus time of V_{GS} is shown in purple.

Results

The long record length allows simultaneous evaluation of the startup behavior and the transition to continuous conducting mode. During the startup phase (2), the gate driver starts at higher frequencies (shown with the track function in purple) to regulate the gain of the LLC converter. However, the controller of the gate driver inserts gaps, which are indicated by a close-to-zero switching frequency. The inrush current (orange) is controlled by the PFC circuit, while the output voltage is ramping up to 24 V (blue) in this phase (4). A steady state is reached after the startup phase. The start frequency and the control loop design influence the time needed to achieve a steady state.

In continuous mode (3), which is achieved after approximately 110 ms, the frequency of the totem pole (half-

bridge) switching circuit shows 100 Hz modulation¹⁾. This indicates variations of the primary rectifier in the DUT. During consumption of the capacitor tank charge in the decreasing half-sine wave, less voltage is offered to the LLC resonant converter. Therefore, the switching frequency needs to be adjusted to vary the gain of the circuit in order to deliver a constant DC voltage at the output of the DUT.

Summary

Analyzing the startup behavior of power converters requires oscilloscopes with deep memory in order to capture the relatively long startup phases and probing solutions for safe measurements on high voltages. Measurement bandwidth is important since switching times are often very short. The probing point for V_{GS} of the high side switch is affected by common mode. High voltage differential probes need to suppress this effect via a good common mode rejection ratio (CMRR). Automated measurement functions in combination with track functionality make it easier to analyze single events (such as power-on) and reveal "long-term" variations such as the internal variation of 100 Hz.

¹⁾ V_{GS} was low pass filtered with a 5 MHz digital filter in order to damp ringing originating from the other transistor Q_2 . This allows a clear switching frequency measurement versus time.



Startup behavior of an LLC resonant converter:

- (1) Zoom of V_{GS} (yellow) and V_{DS} (green)
- (2) Switching frequency of V_{GS} versus time during startup
- (3) Switching frequency during conducting mode of approx. 120 kHz with 100 Hz modulation
- (4) Inrush current I_{in} (orange) and output voltage V_{out} (blue) of the power supply.

Rohde & Schwarz GmbH & Co. KG

Europe, Africa, Middle East | +49 89 4129 12345
 North America | 1 888 TEST RSA (1 888 837 87 72)
 Latin America | +1 410 910 79 88
 Asia Pacific | +65 65 13 04 88
 China | +86 800 810 82 28 | +86 400 650 58 96
 www.rohde-schwarz.com
 customersupport@rohde-schwarz.com

R&S® is a registered trademark of Rohde&Schwarz GmbH&Co. KG
 Trade names are trademarks of the owners
 PD 5216.1757.92 | Version 01.00 | November 2018 (he)
 Measuring power-on behavior of LLC resonant converters
 Data without tolerance limits is not binding | Subject to change
 © 2018 Rohde&Schwarz GmbH&Co. KG | 81671 Munich, Germany



5216175792