




# Agenda


- System Overview
  - Test Setup and Equipment
  - Test Specification
  - Demo Objectives
- Test #1: Time Domain Impact of RC Snubber
- Test #2: Reference Measurement (No filtering)
- Test #3: Test #2 + RC Snubber
- Test #4: Test #3 + Pri->Sec Caps
- Test #5: Test #4 + {CMC + i/p Y-Caps}




# System Overview

## Test Setup & Equipment

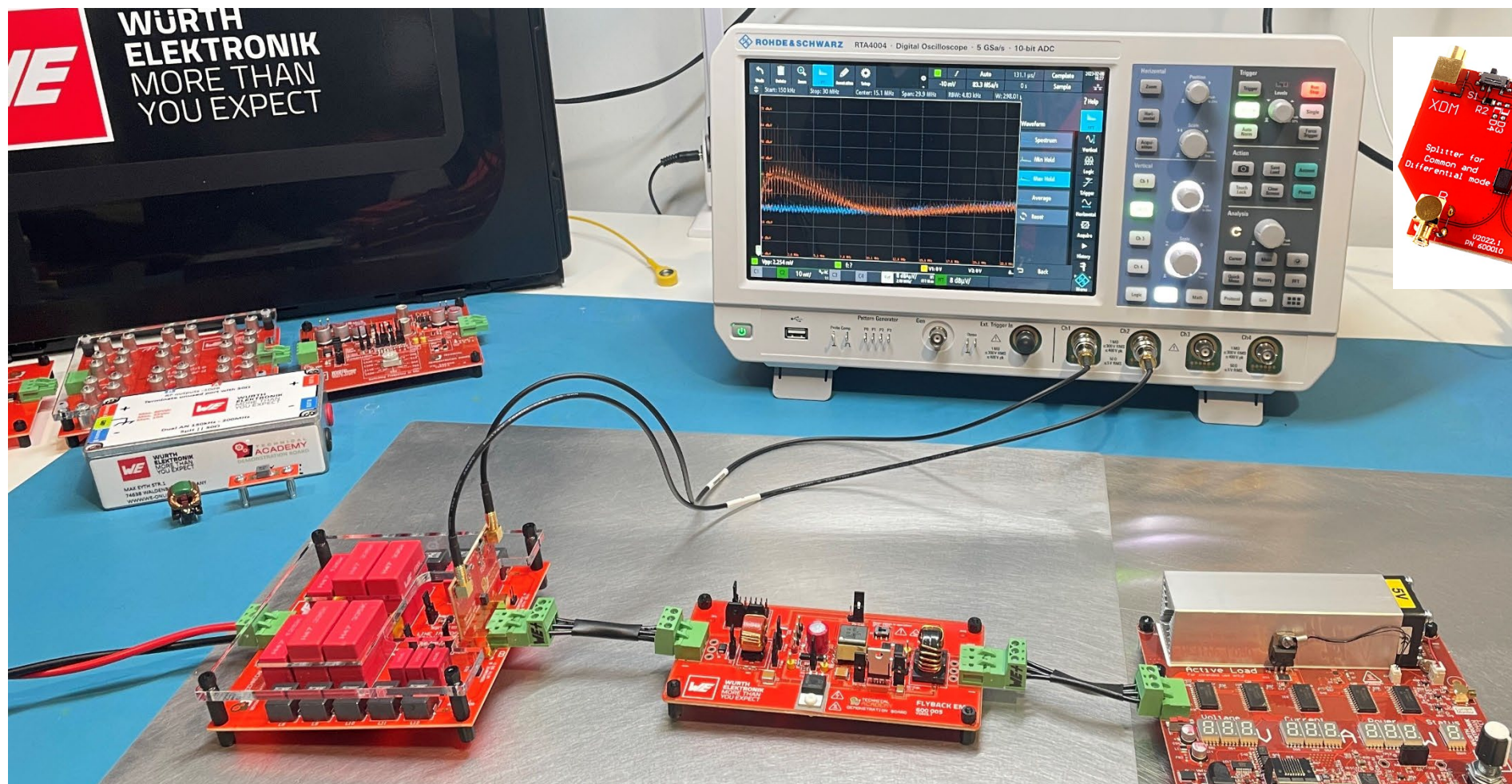

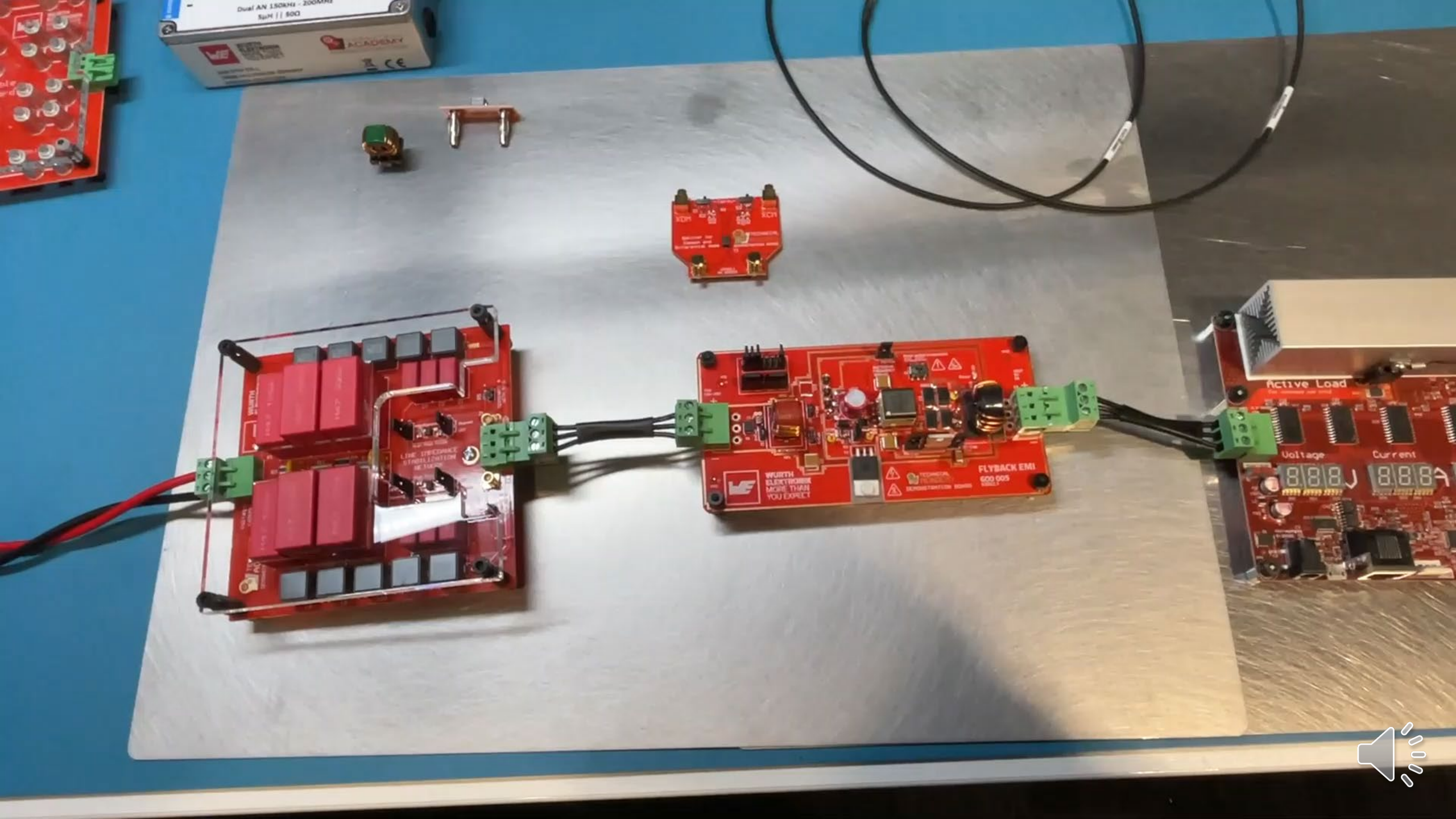


Dual AN 150kHz - 200MHz  
SpM II 500

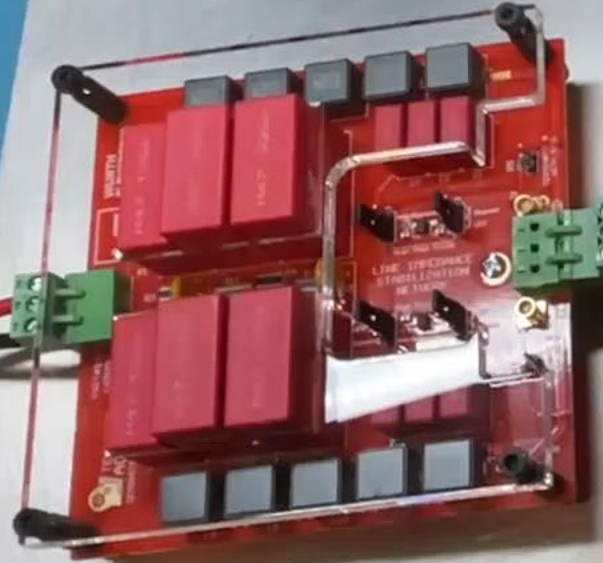


# System Overview
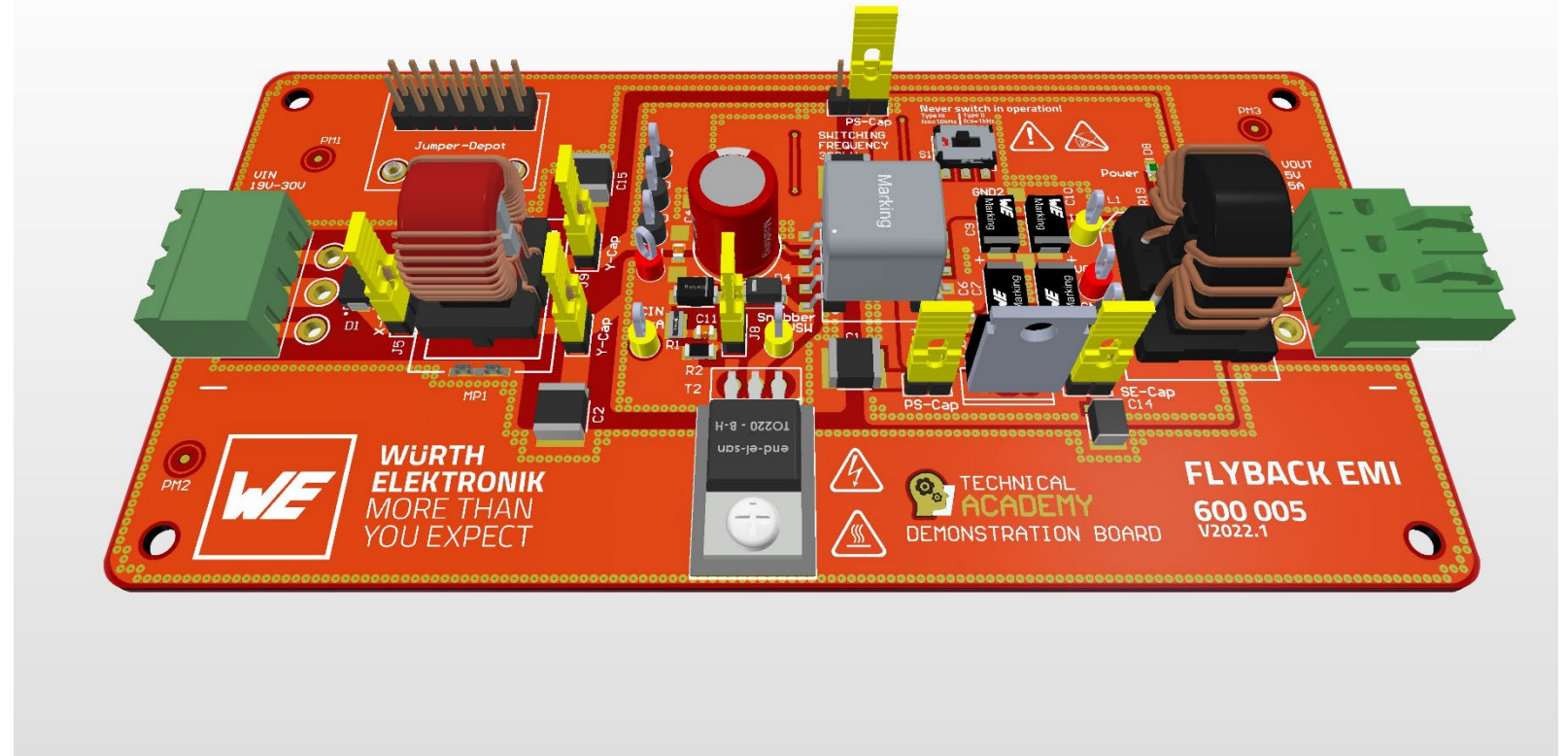
## Test Specifications

- DC/DC Flyback-Converter CCM (Continuous Conduction Mode)
  - $U_{in} = 24V$  (19-30V)
  - $U_{out} = 5V$
  - $I_{out,max} = 5A$  (25W)
  - $f_{sw} \approx 300kHz$
  - Efficiency  $\approx 90\%$
- IC: ADP1071-2 (Analog Devices)
  - with synchronous rectifier
- Transformer: 749119550
- MOSFETs in TO220-package



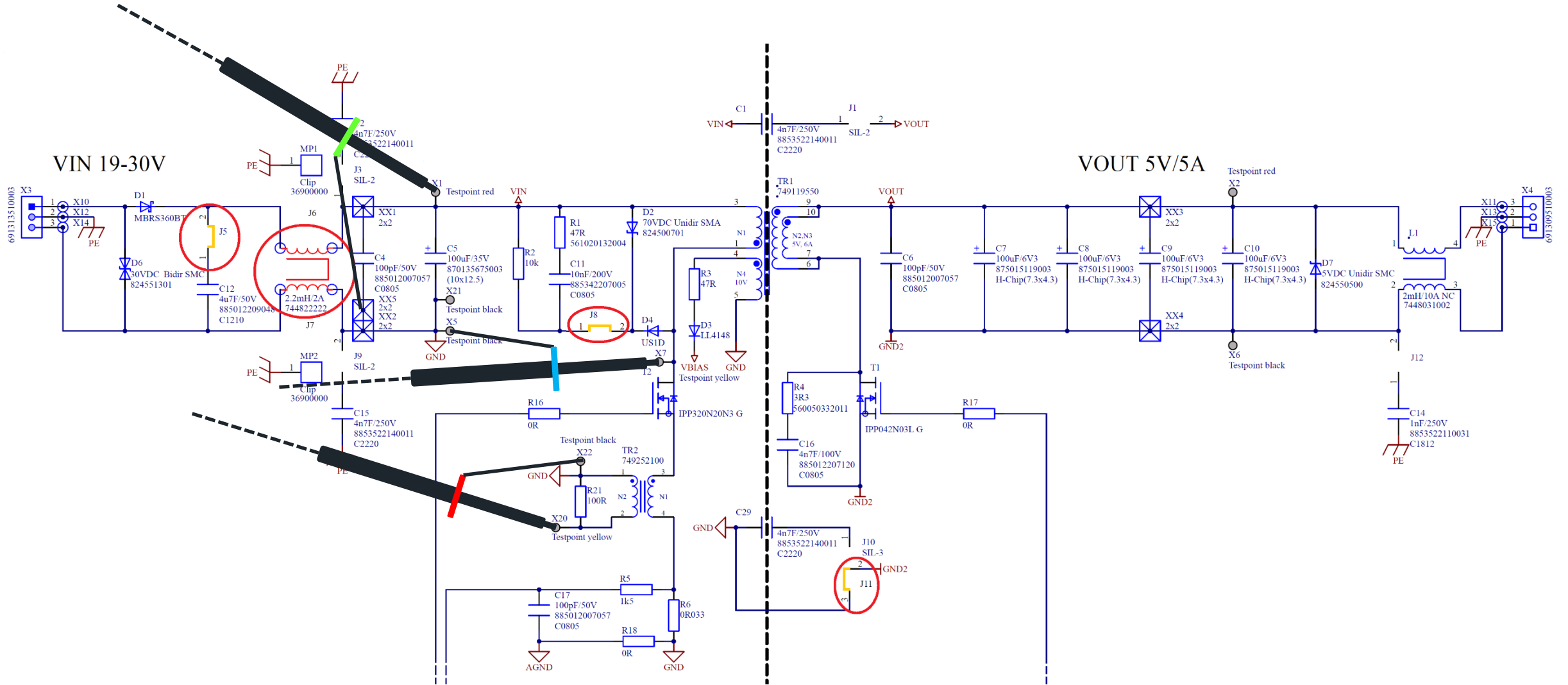
# Test#1: Time Domain Impact of RC Snubber - Schematic





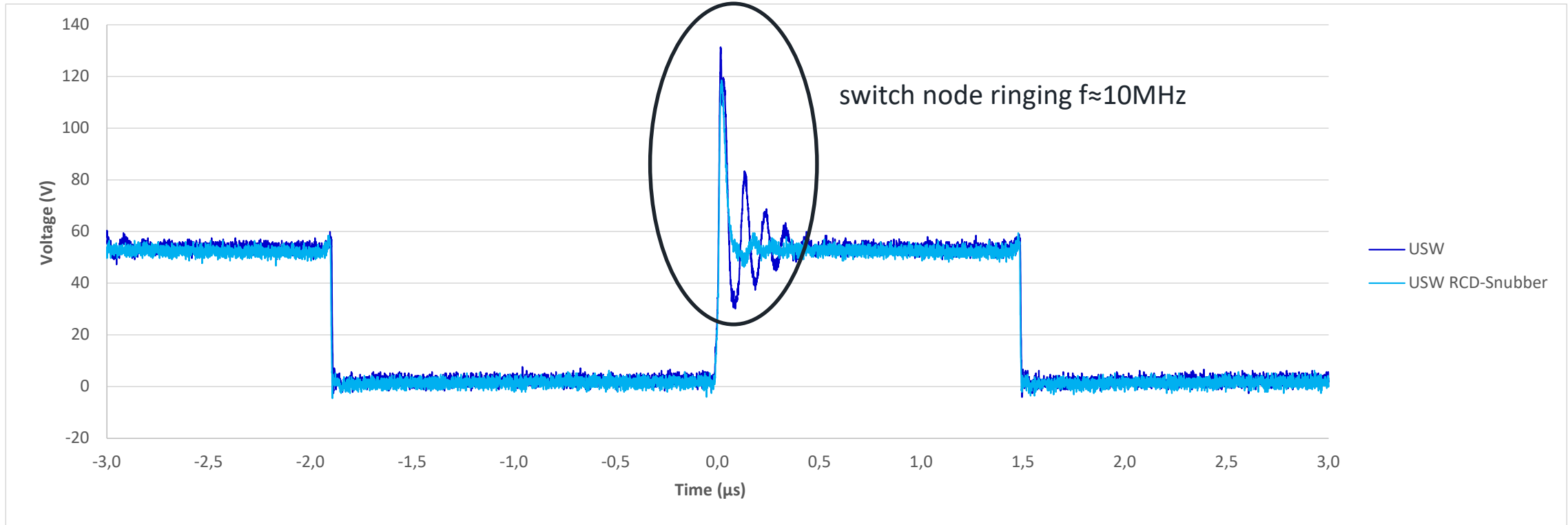
# Test#1: Waveforms - switch node voltage






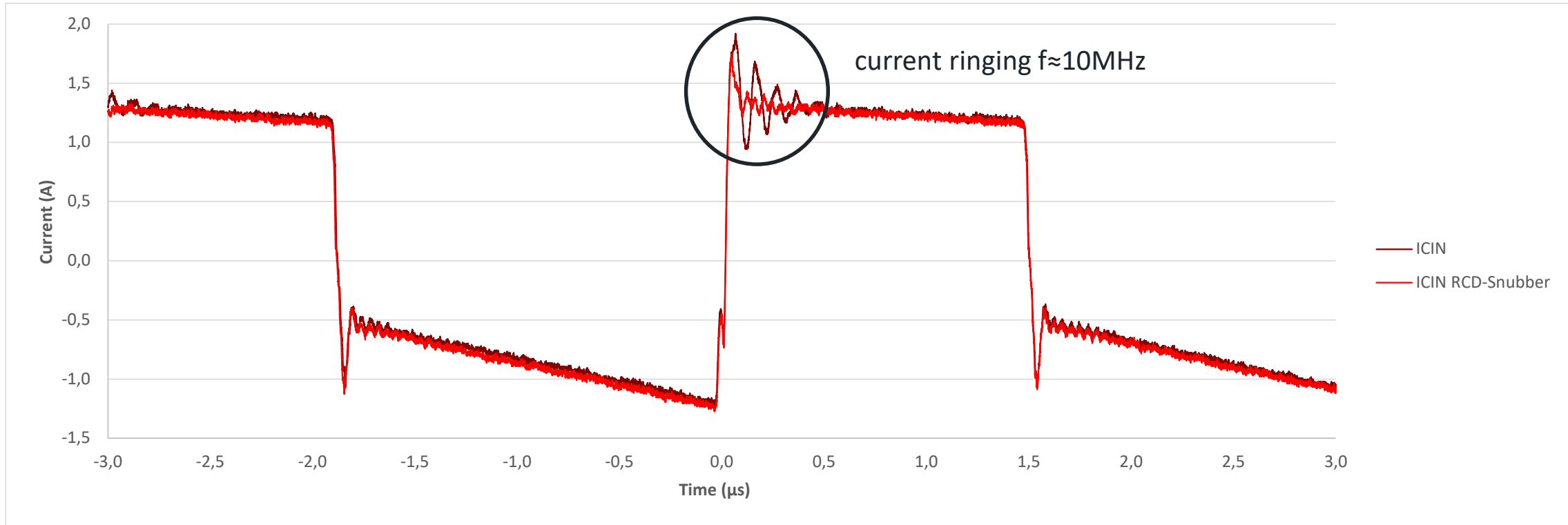
# Test#1: Waveforms - input capacitor current


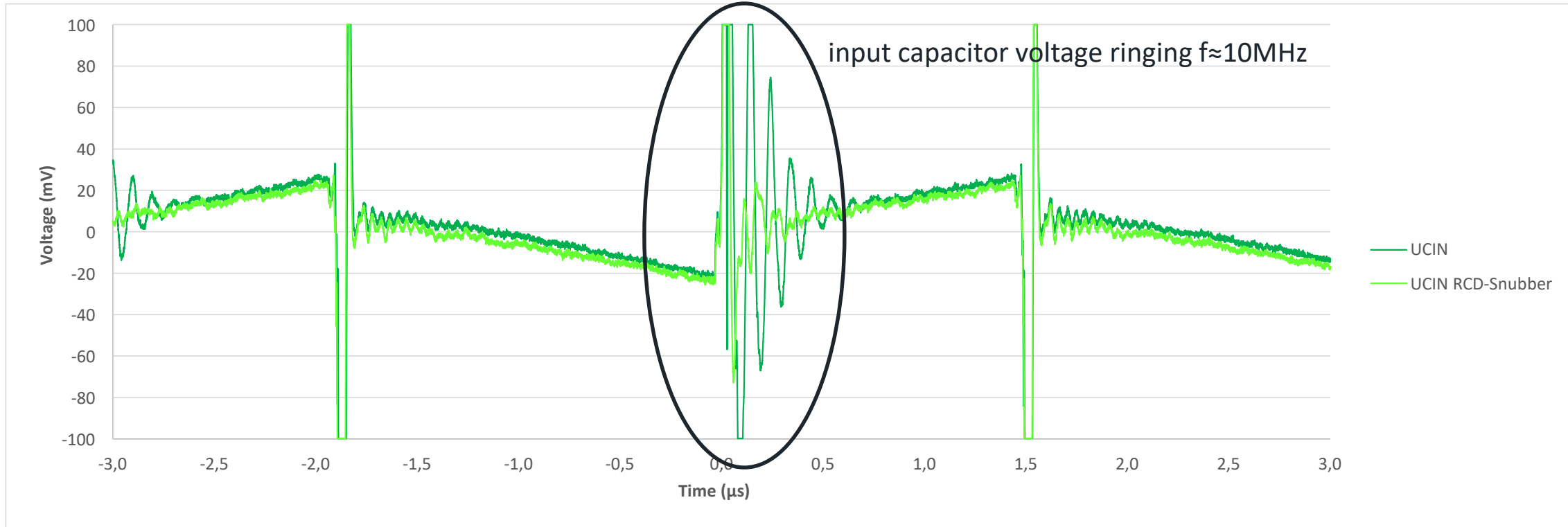
# Test#1: Waveforms – input capacitor voltage AC



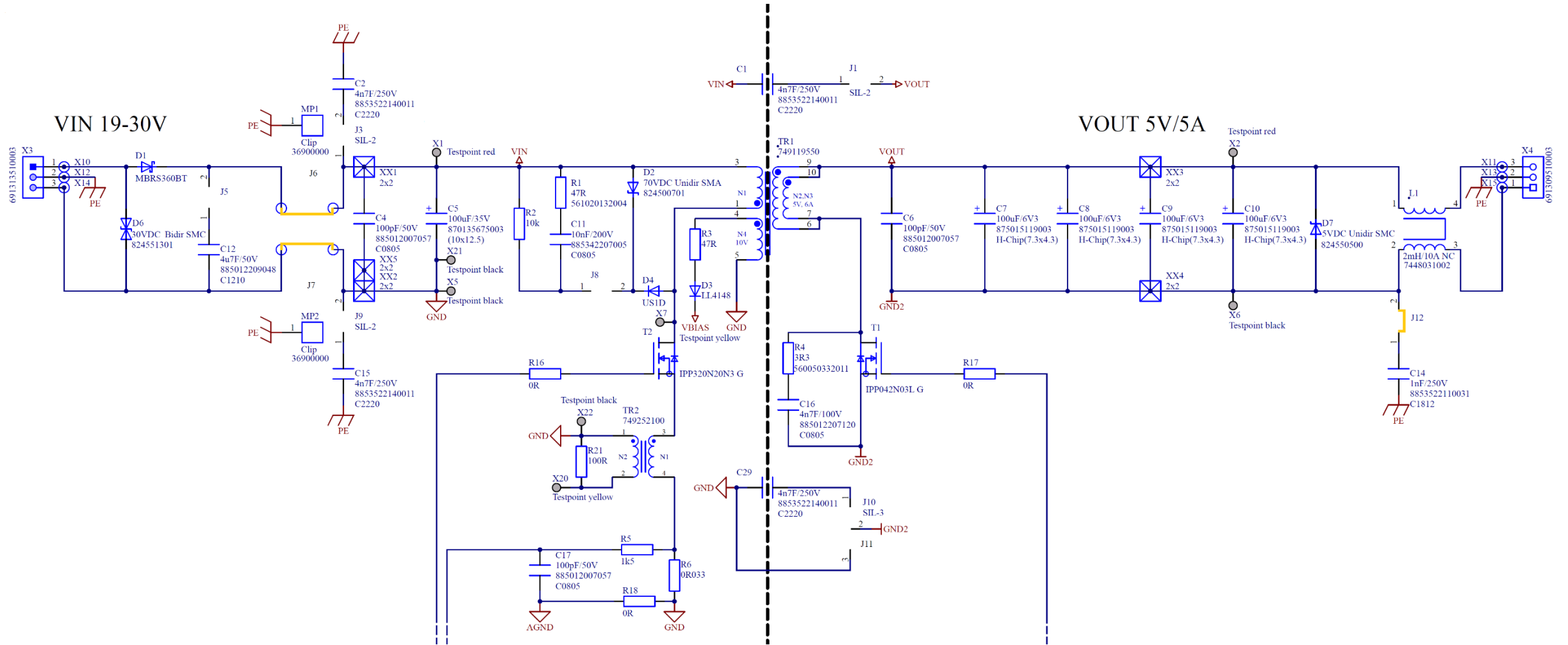
# Test#2: Reference Measurement - Schematic





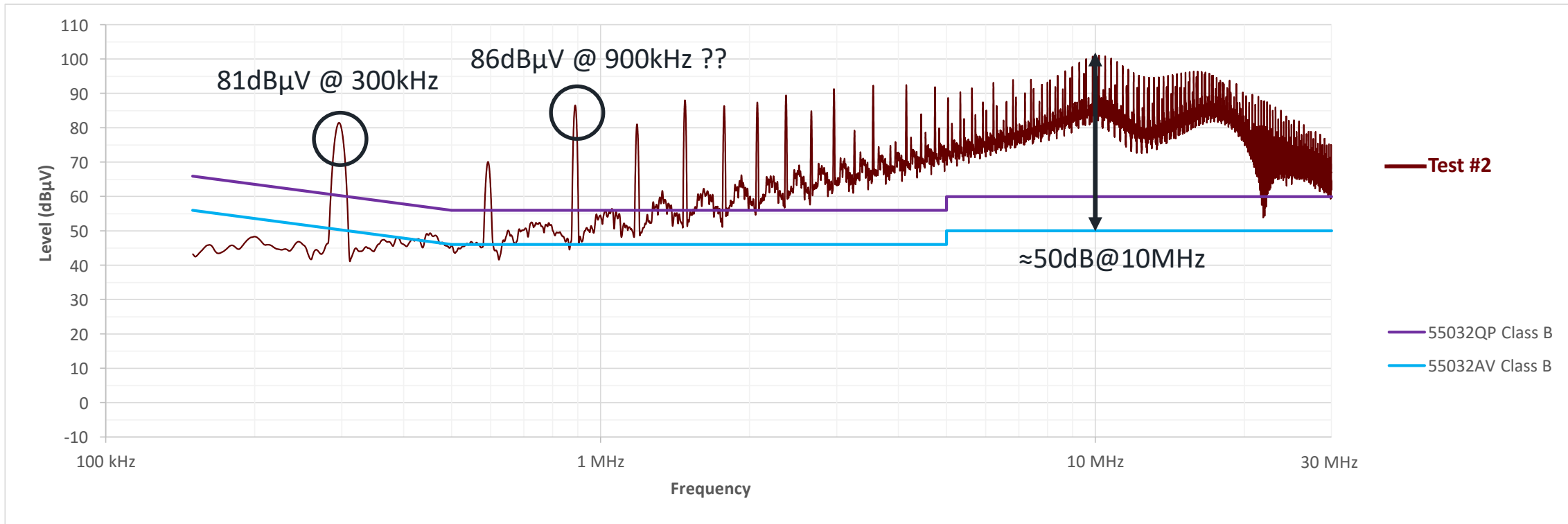
## Test#2: Total conducted emissions – Line



Name	Description
<b>Test #2</b>	Reference (no improvement)

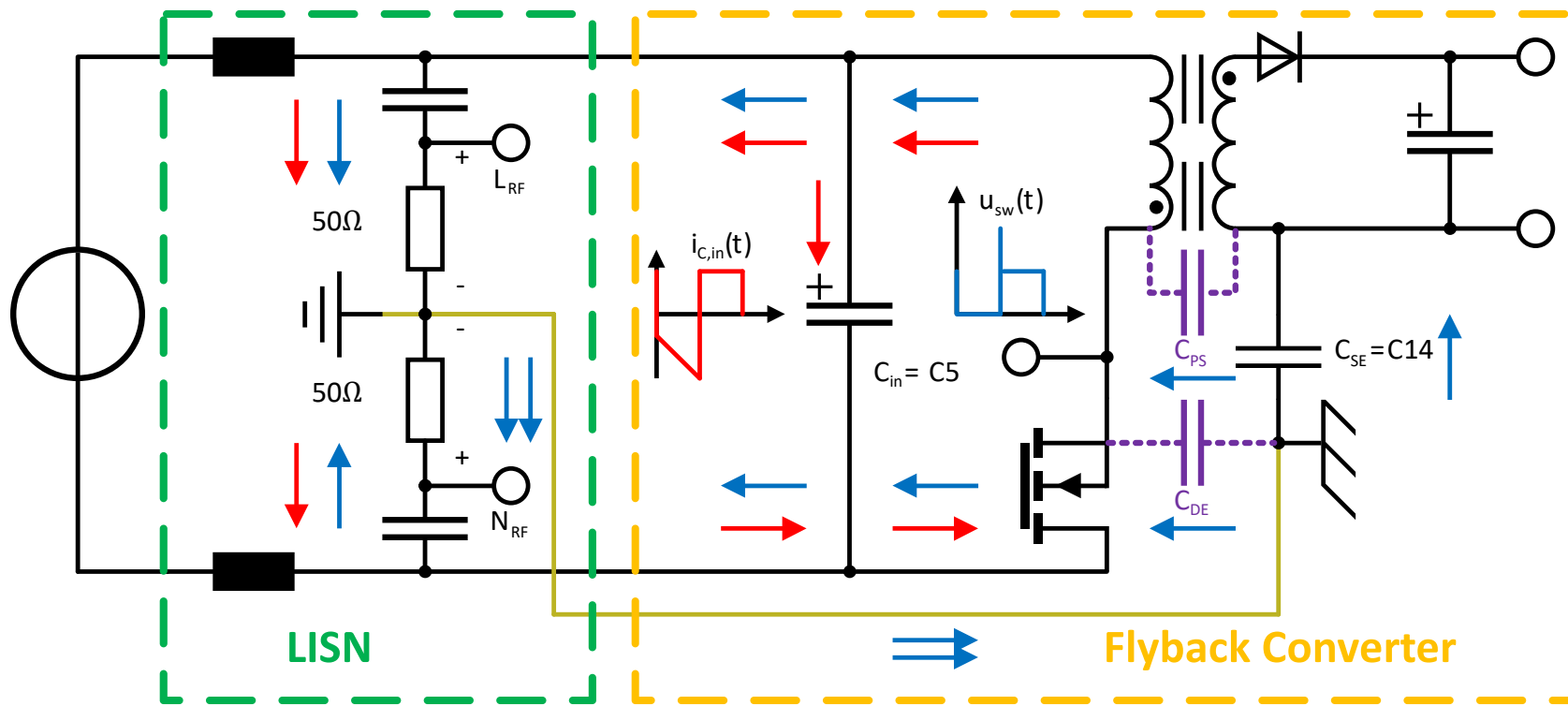
# Test#2: Background

Theory: DM and CM noise path in a flyback converter



$$U_{L,RF} = U_{CM} + U_{DM}$$

$$U_{N,RF} = U_{CM} - U_{DM}$$

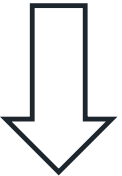

$$U_{DM} = \frac{U_{L,RF} - U_{N,RF}}{2}$$


$$U_{CM} = \frac{U_{L,RF} + U_{N,RF}}{2}$$

→ DM Current      PE-Frame      PE = Reference Ground  
→ CM Current

MaT/eiSos


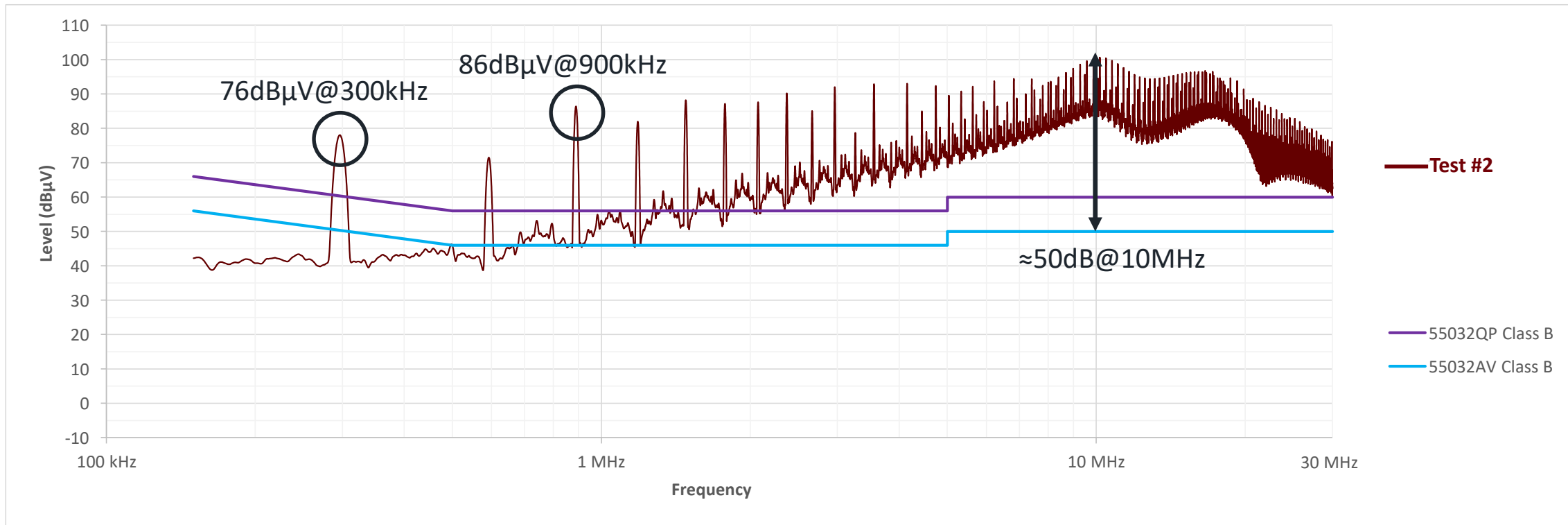
## Test#2: Conducted emissions - Common mode



Name	Description
Test #2	Reference (no improvement)




Horizontal: Zoom, Horizontal, Acquisition, Vertical (FFT), Ch 2, Ch 3, Ch 4, Logic, Ref, Math. Trigger: Trigger, Levels, Single, Auto Norm, Force Trigger. Action: Camera, Save Load, Autoast, Touch Lock, Clear Screen, Preset. Analysis: Cursor, Measure, Quick Measure, History, FFT, Protocol, Gen.

Pattern Generator, Gen, Ext. Trigger In, Ch1, Ch2, Ch3, Ch4. Includes a power button, USB port, and various input connectors with technical specifications.



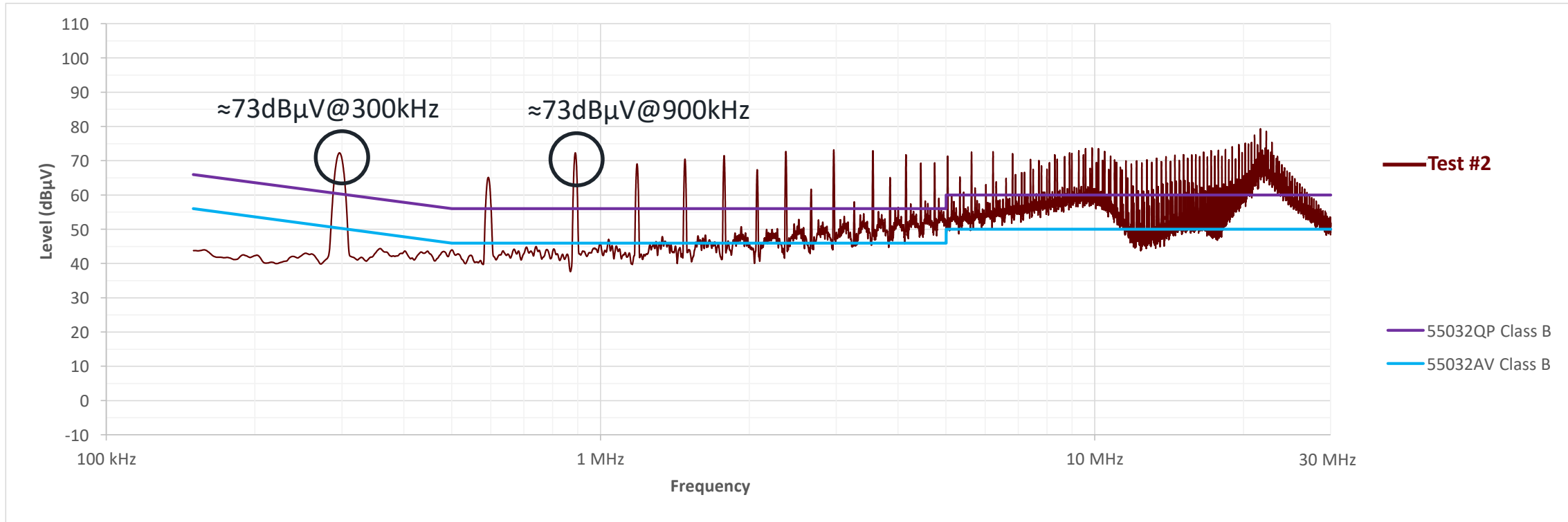
## Test#2: Conducted emissions - Differential mode




Name	Description
<b>Test #2</b>	<b>Reference (no improvement)</b>




# Test#3: Board configuration

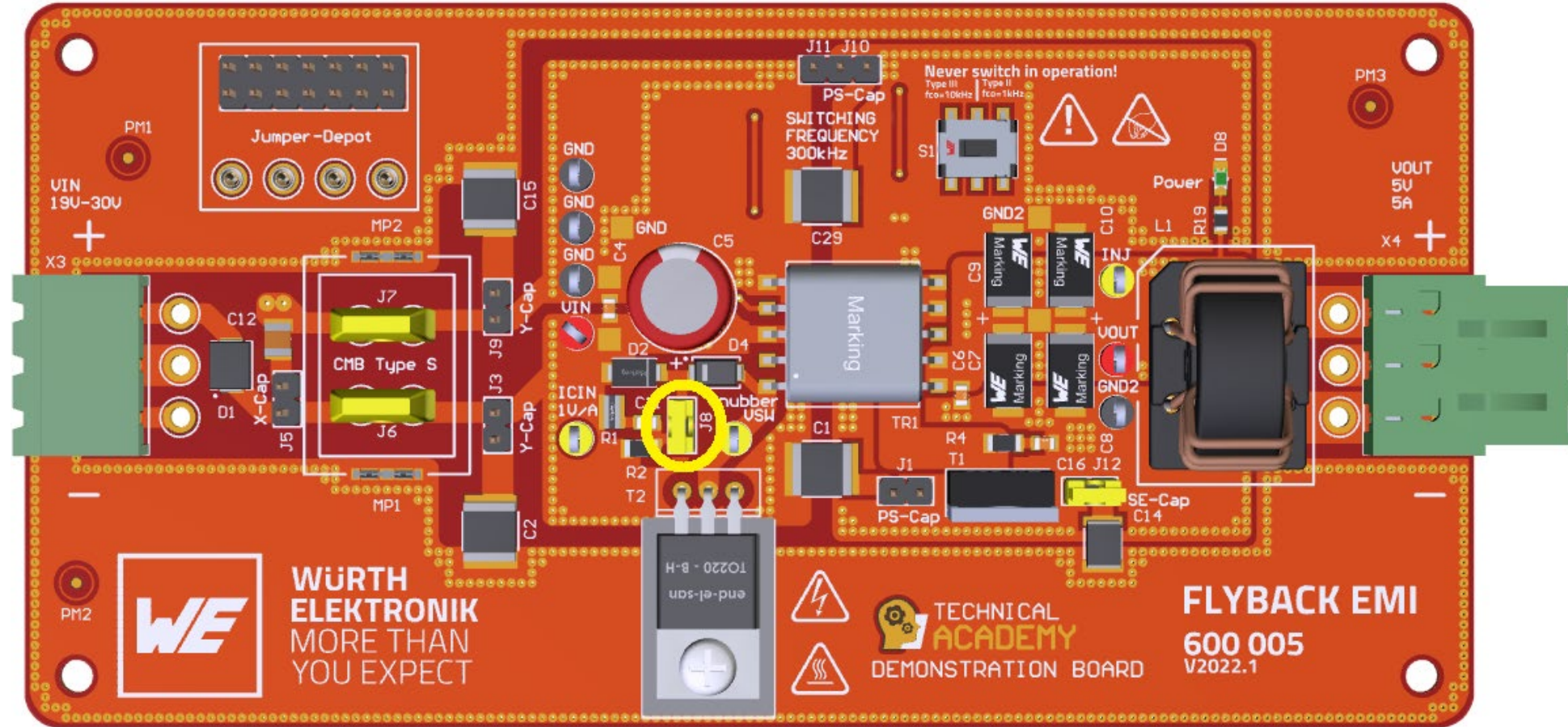
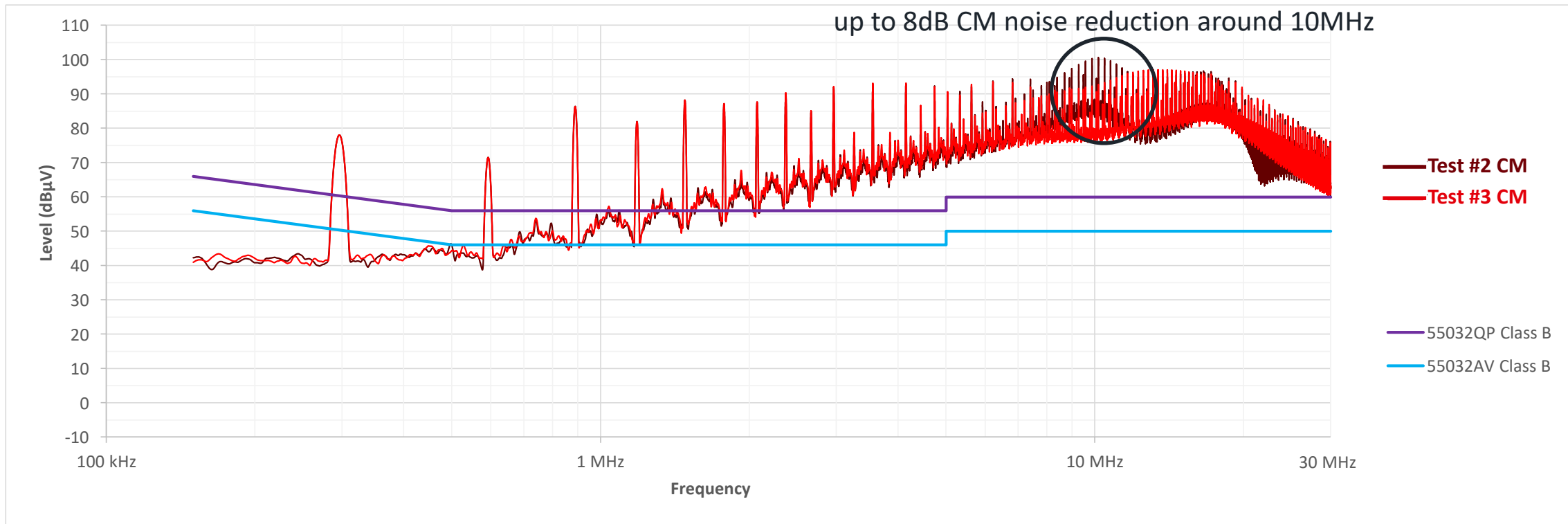
## Test#3: Conducted emissions - Common mode



Name	Description
Test #2	Reference (no improvement)
Test #3	Test#2 + RCD-snubber

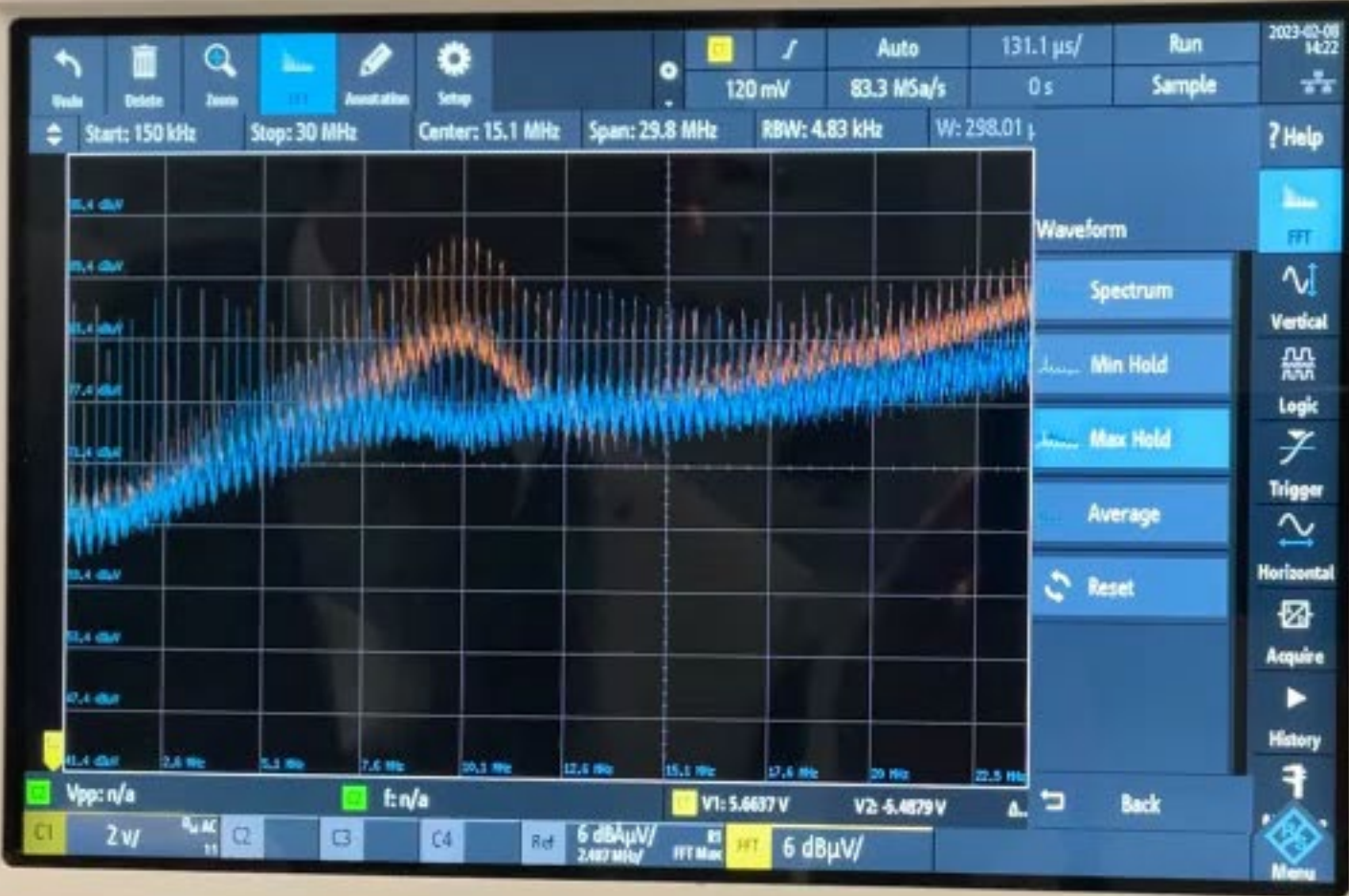

Physical control panel with the following sections:


- Horizontal:** Zoom knob, Horizontal knob, Acquisition knob.
- Vertical:** Vertical knob, Ch 2, Ch 3, Ch 4 buttons, Scale knob.
- Trigger:** Trigger, Levels knob, Run Stop, Single, Force Trigger buttons.
- Action:** Camera, Save Load, Autoreset, Touch Lock, Clear Screen, Preset buttons.
- Analysis:** Cursor knob, Menu, FFT, Protocol, Gen buttons.
- Other:** Logic, Math buttons.

Front panel connectors and controls:

- Power button (green)
- USB port
- Probe Comp. section
- Pattern Generator (PG) with P1, P2, P3 outputs
- Gen (Generator) output
- Ext. Trigger In with 1 MΩ and 50 Ω termination options
- Ch1, Ch2, Ch3, Ch4 input connectors with specifications: 1 MΩ ≤ 300 V RMS ≤ 400 V pk, 50 Ω ≤ 5 V RMS



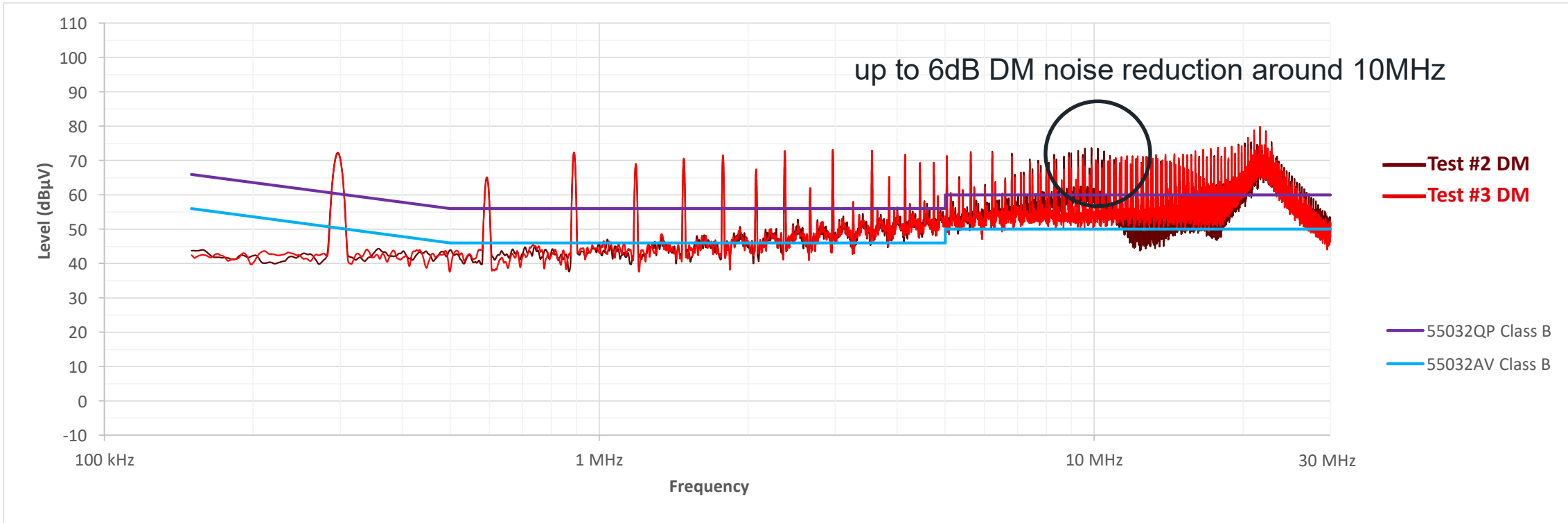
# Test#3: Conducted emissions - Differential mode



Name	Description
Test #2	Reference (no improvement)
Test #3	Test#2 + RCD-snubber

## Test#3: Background


### Common mode

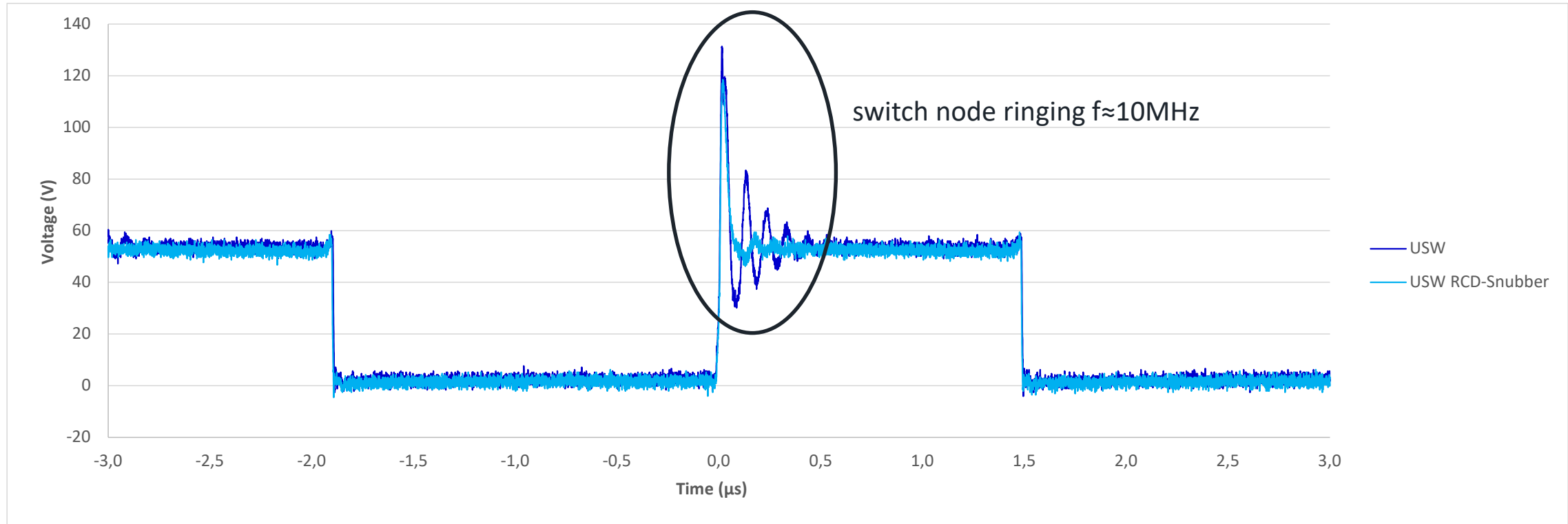

- The voltage change at the switch node is the cause of the CM noise
- The 10MHz switch node ringing is damped by the snubber

## Test#3: Background


Differential mode

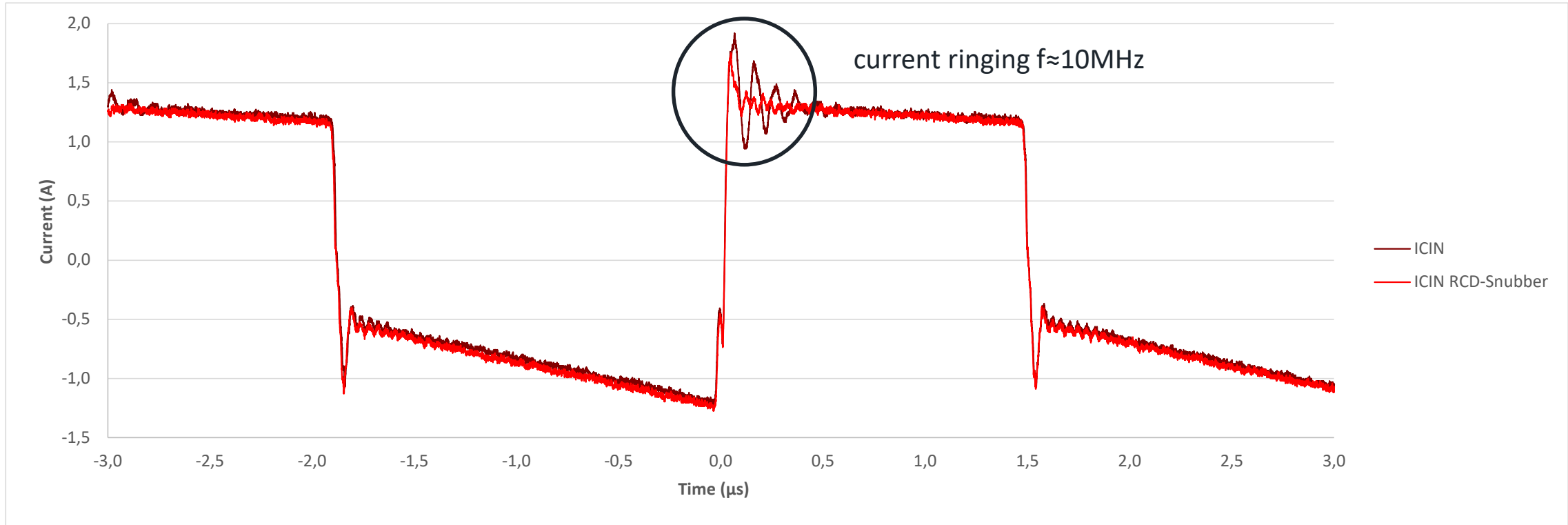


- The input capacitor current waveform causes a voltage drop across the impedance of the input capacitor
- The 10MHz current ringing is damped by the snubber




# Test#4: Pri -> Sec Caps - Schematic

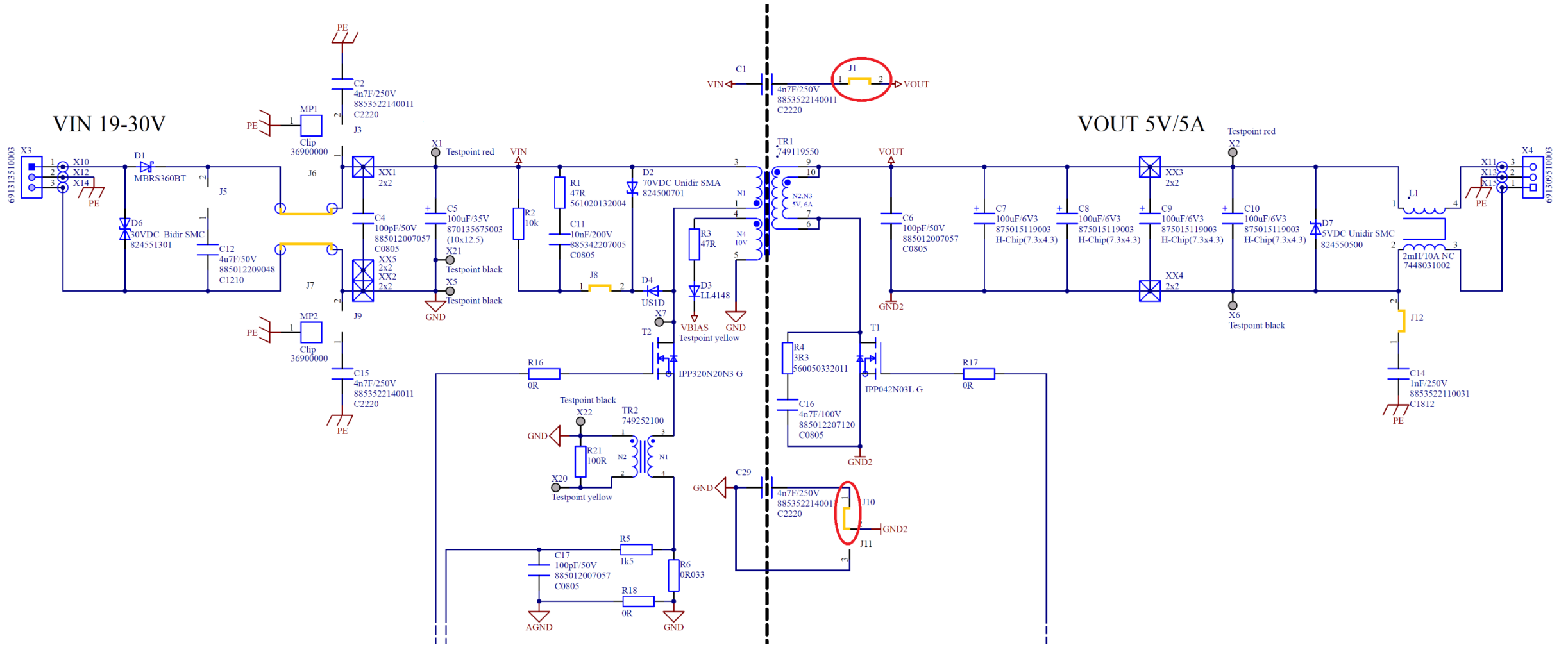

# Test#4: Board configuration

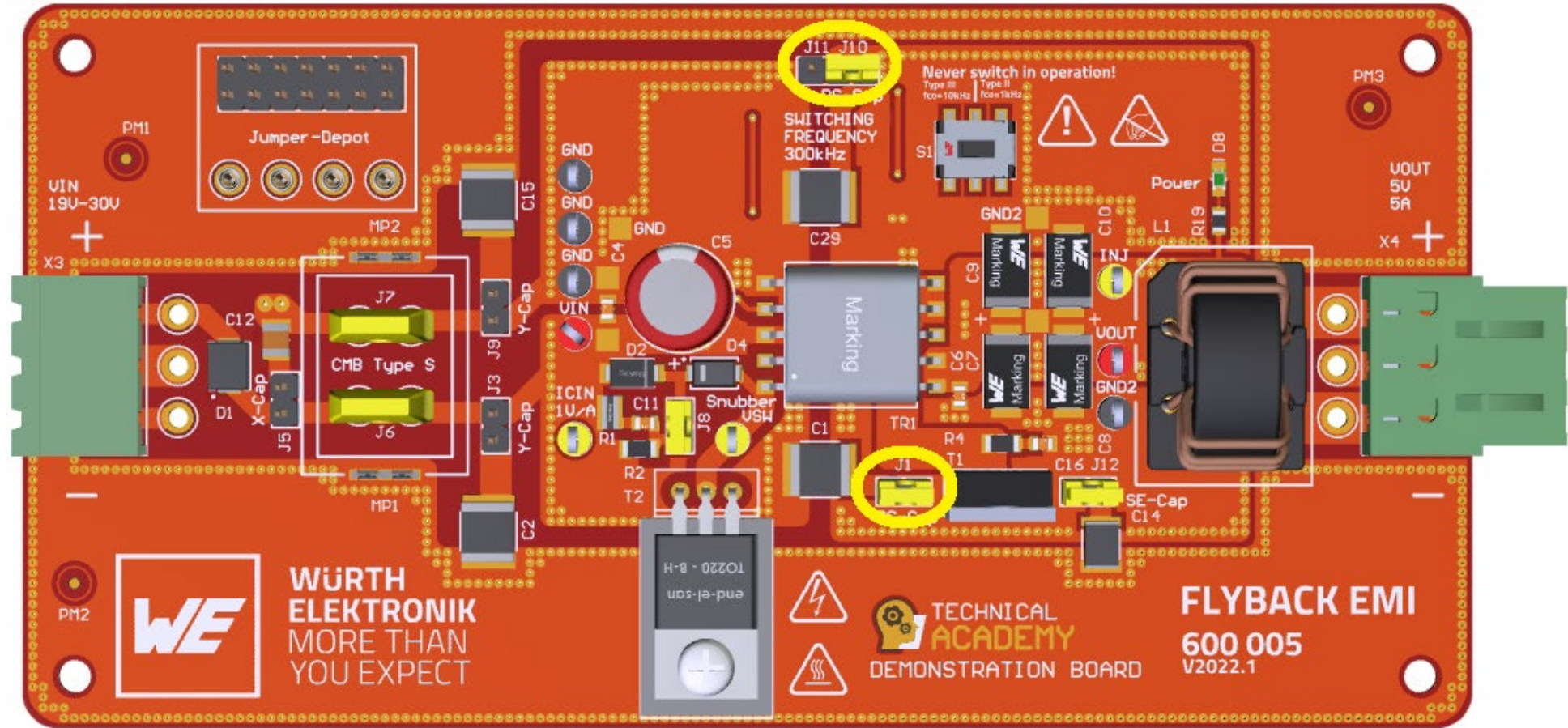

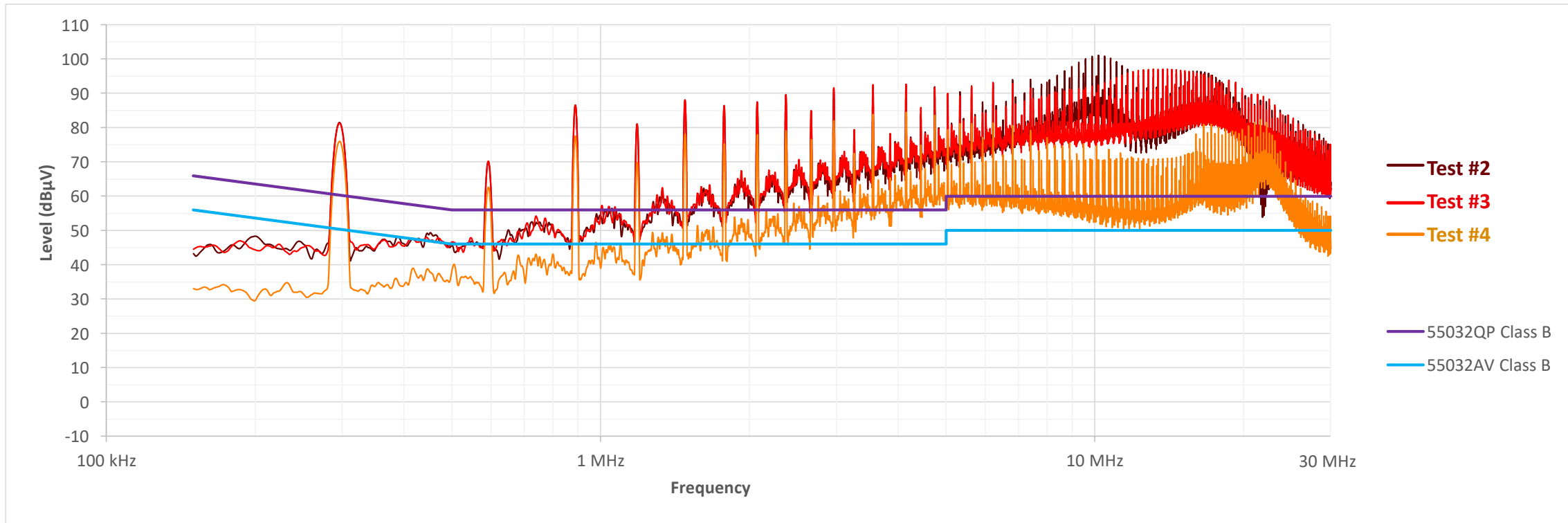
## Test#4: Total conducted emissions - Line



Name	Description
Test#2	Reference (no improvement)
Test#3	Test#2 + RCD-snubber
Test#4	Test#3 + primary to secondary y-capacitors
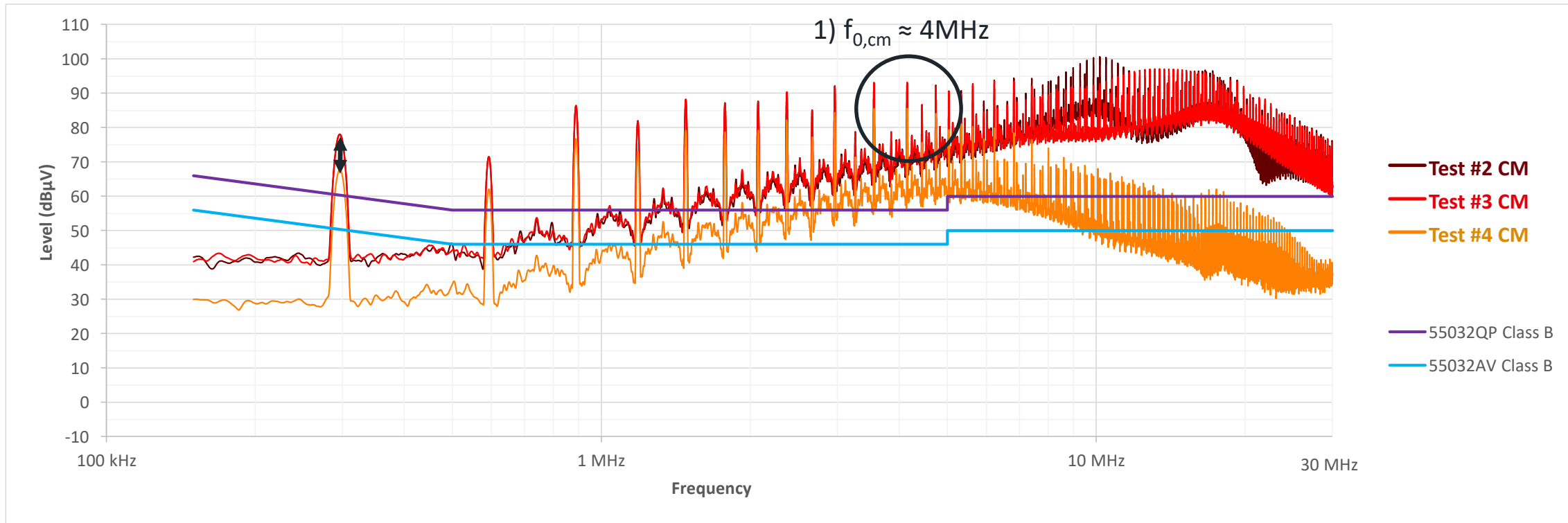
## Test#4: Conducted emissions - Common mode




Name	Description
Test#2	Reference (no improvement)
Test#3	Test#2 + RCD-snubber
Test#4	Test#3 + primary to secondary y-capacitors

## Test#4: Background

Measurement: 1) CM line inductance L/N & PE




$$L_{cm,L/N} \approx 0,8\mu H$$

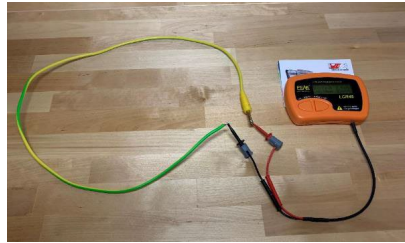

$$L_{PE} \approx 0,8\mu H$$

$$\rightarrow L_{line} = L_{PE} + L_{cm,L+N} \approx 0,8\mu H + 0,8\mu H = 1,6\mu H$$

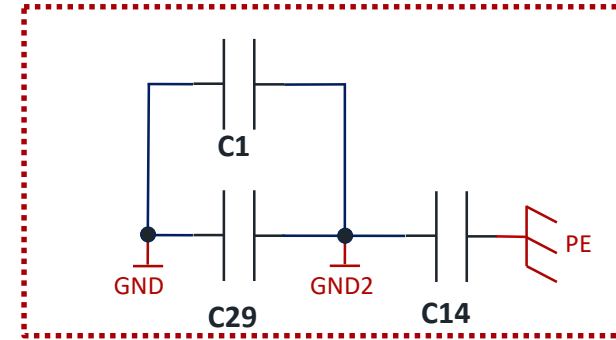
Effective ground capacitance in common mode




$$\rightarrow C_E \approx \frac{(C_1 + C_{29}) \cdot C_{14}}{C_1 + C_{29} + C_{14}} = \frac{(4,7nF + 4,7nF) \cdot 1nF}{4,7nF + 4,7nF + 1nF} \approx 0,904nF$$

$$f_{0,cm} = \frac{1}{2\pi \cdot \sqrt{L_{line} \cdot C_E}} = \frac{1}{2\pi \cdot \sqrt{1,6\mu H \cdot 0,904nF}} \approx 4,2MHz$$


# Test#5: CMC + i/p Y-Caps - Schematic

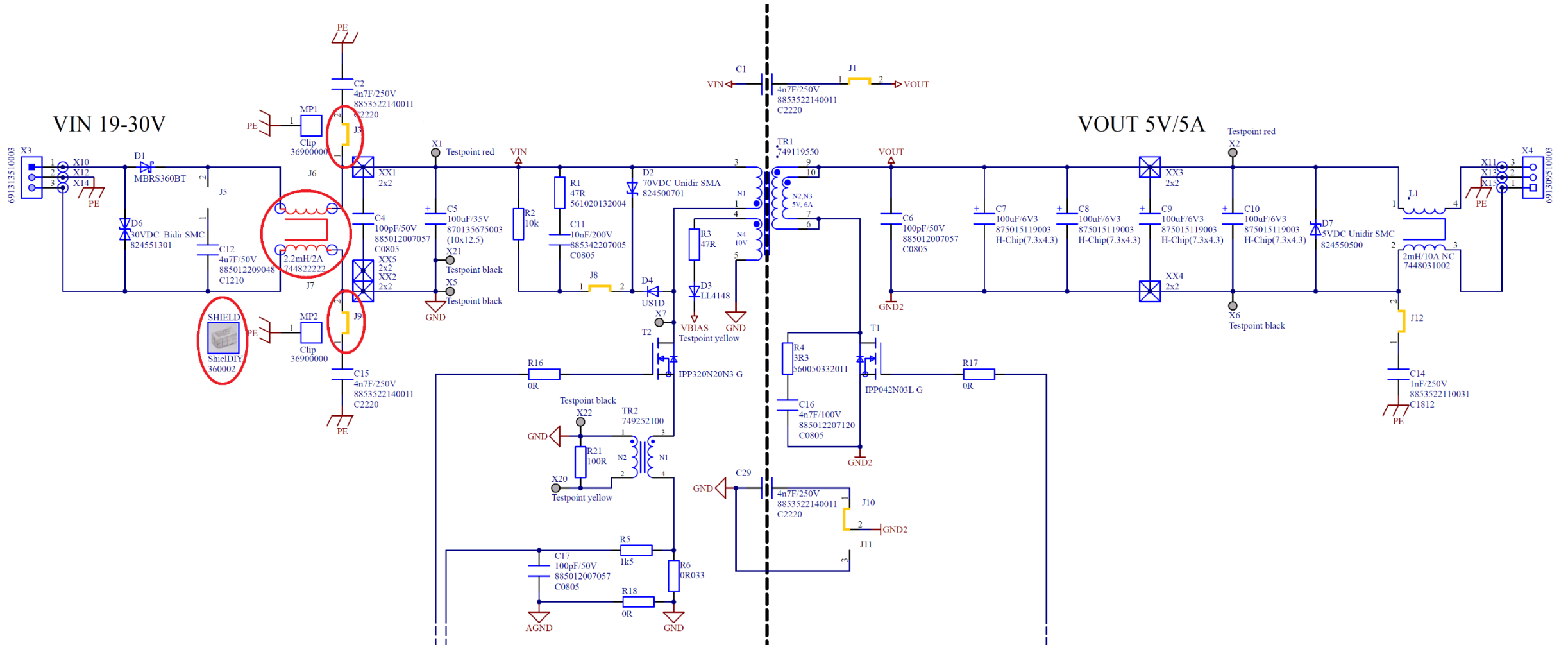

# Test#5: Board configuration

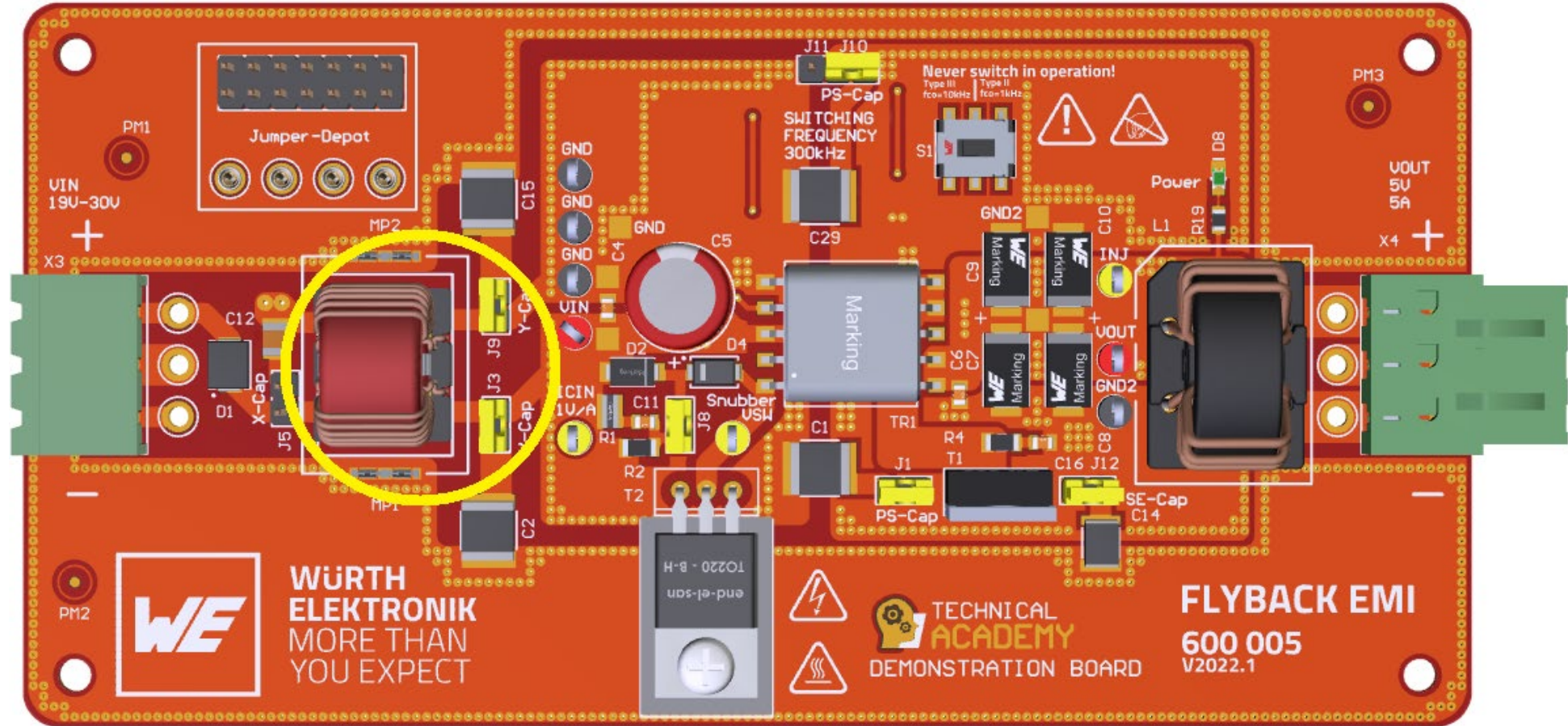

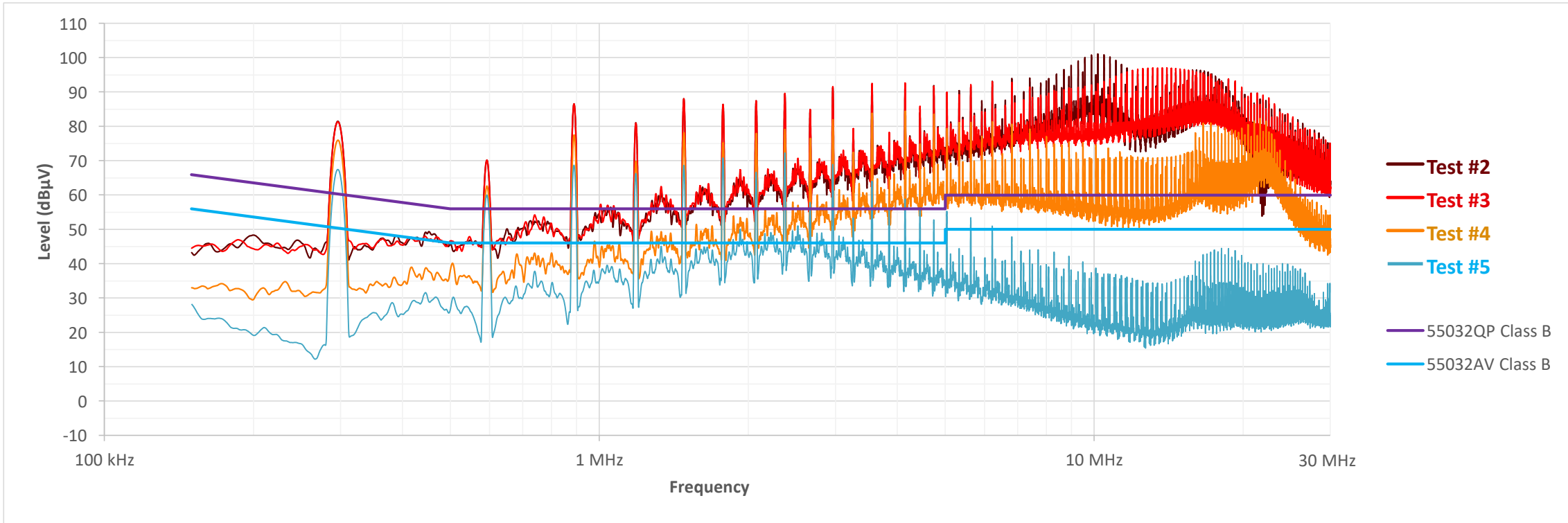
# Test#5: Total conducted emissions – Line



Name	Description
Test#2	Reference (no improvement)
Test#3	Test#2 + RCD-snubber
Test#4	Test#3 + primary to secondary y-capacitors
Test#5	Test#4 + CMC and y-capacitors (CM filter)



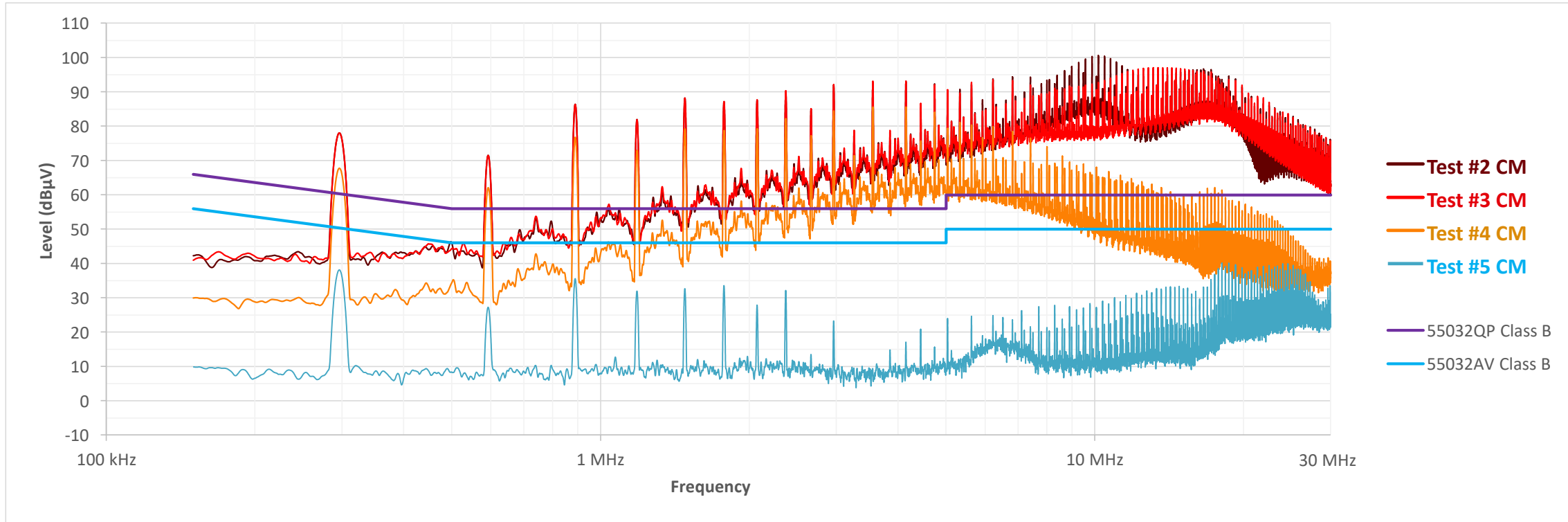
## Test#5: Conducted emissions - Common mode



Name	Description
Test#2	Reference (no improvement)
Test#3	Test#2 + RCD-snubber
Test#4	Test#3 + primary to secondary y-capacitors
Test#5	Test#4 + CMC and y-capacitors (CM filter)

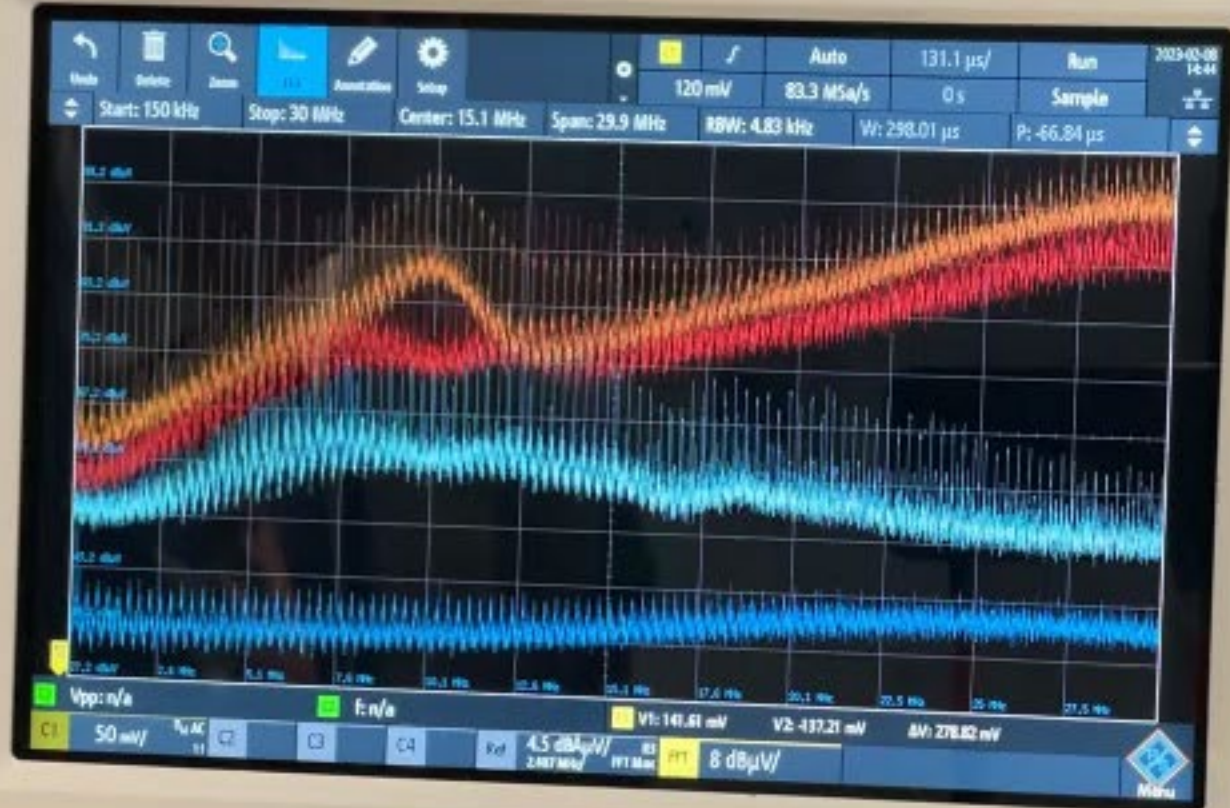ROHDE & SCHWARZ RTA4004 · Digital Oscilloscope · 5 GSa/s · 10-bit ADC



Horizontal

Zoom, Horizontal, Acquisition

Vertical

Ch 2, Ch 3, Ch 4

Logic, Math

Trigger

Trigger, Levels, Single, Force Trigger

Action

Save Last, Auto Zoom, Touch Lock, Clear Screen, Print

Analysis

Cursor, Wave, FFT, Protocol, Gen

Pattern Generator

Probe Comp., P1, P2, P3

Gen

Ext. Trigger In


Ch1, Ch2, Ch3, Ch4

1 M $\Omega$   $\leq$  300 V RMS  $\leq$  400 V pk

50  $\Omega$   $\leq$  5 V RMS


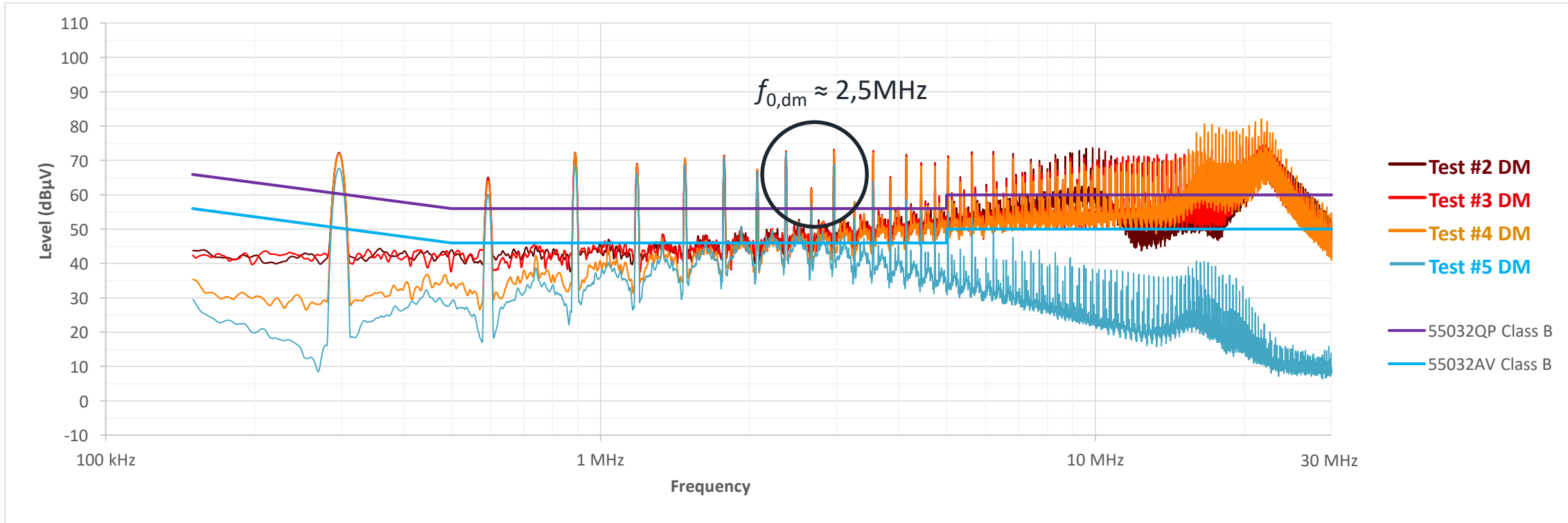
## Test#5: Conducted emissions - Differential mode





Name	Description
Test#2	Reference (no improvement)
Test#3	Test#2 + RCD-snubber
Test#4	Test#3 + primary to secondary y-capacitors
Test#5	Test#4 + CMC and y-capacitors (CM filter)

Where does this cut off frequency come from?  
How do we attenuate this DM noise?

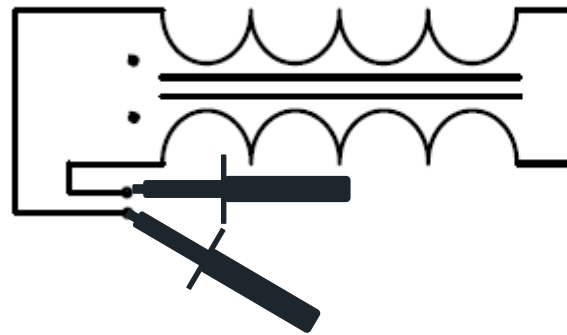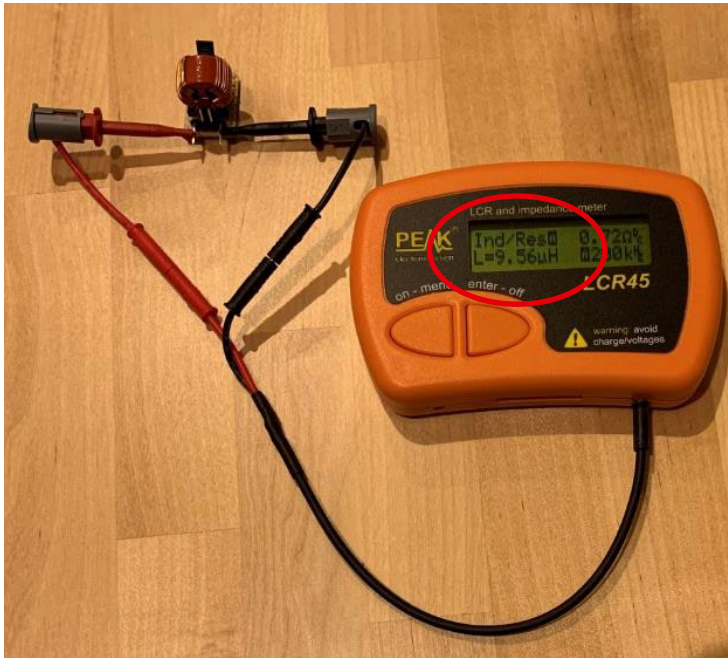
## Test#5: Background

Measurement: Stray inductance

- The stray inductance of the CMC and the junction capacitance ( $C_{J,D6} \approx 400pF$ ) of D6 (WE-TVSP) act as differential mode filter (LC-filter) for free
  - Stray inductance of the CMC (744822222 – 2.2mH/2A CMB Type S):



$$L_{S,cmc} \approx 10\mu H$$

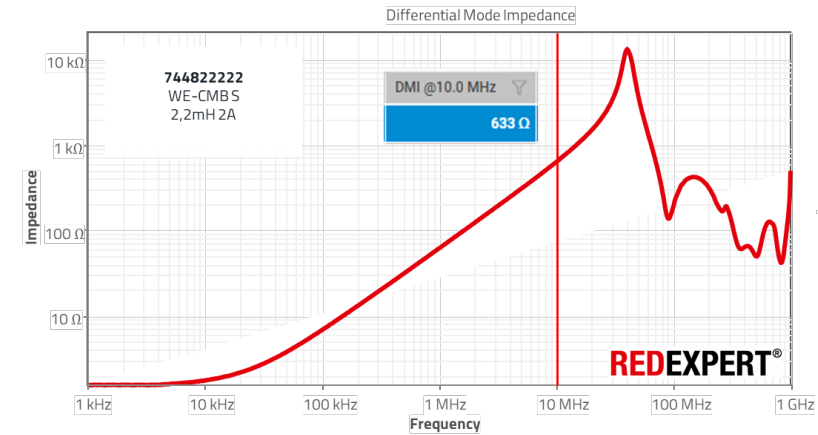

$$L_{S,cmc} = L_{dm} = \frac{|Z_{dm}|}{2\pi \cdot f} = \frac{633\Omega}{2\pi \cdot 10MHz} \approx 10\mu H$$

$$f_{0,dm} = \frac{1}{2\pi \cdot \sqrt{L_{S,cmc} \cdot C_{J,D6}}} = \frac{1}{2\pi \cdot \sqrt{10\mu H \cdot 400pF}} \approx 2,5MHz$$

